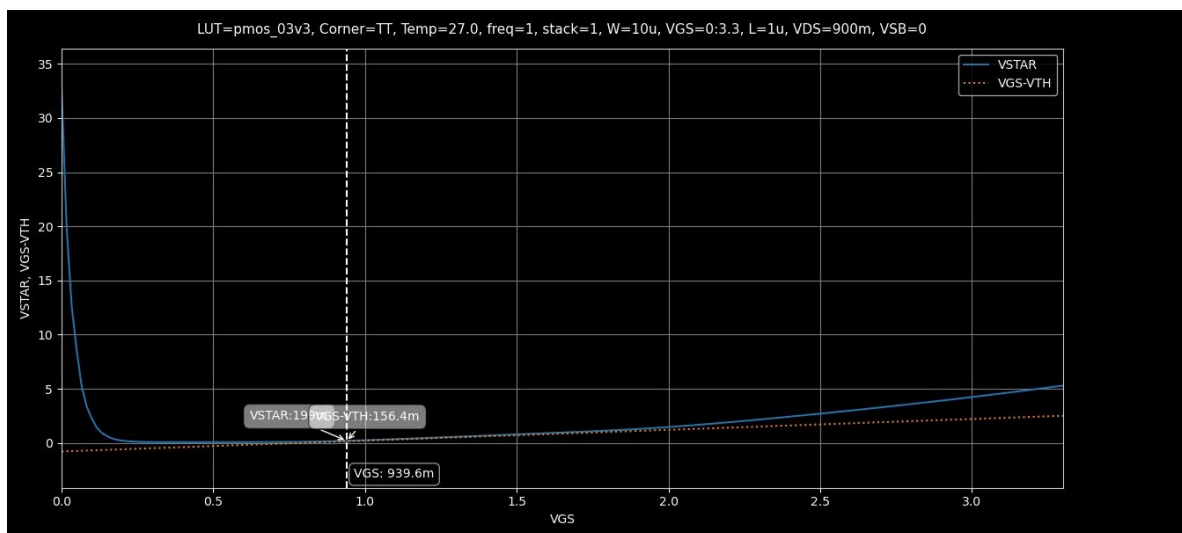


CMOS AIC design - ITI - Lab 4

Part 1: Sizing Chart Using ADT SA


- An often used sweet-spot that provides good compromise between different trade-offs is $V^* = 200mV$. On the V^* and V_{ov} chart locate the point at which $V^* = 200mV$. Find the corresponding V_{ovQ} and V_{GSQ} .



V^* and V_{ov} vs V_{GS}

$$V_{ovQ} \approx 160mV, V_{GSQ} \approx 940mV.$$

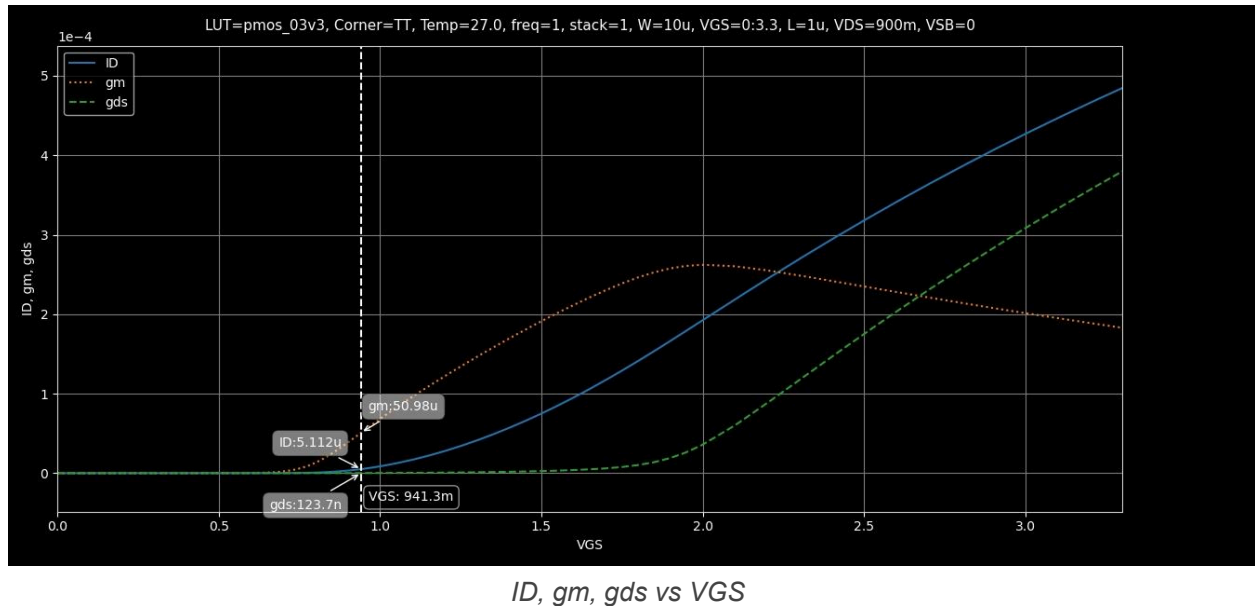- Plot I_D , g_m and g_{ds} vs V_{GS} . Find their values at V_{GSQ} . Let's name these values I_{DX} , g_{mX} and g_{dsX} .



$$I_{DX} \approx 5\mu A, g_{mX} \approx 50\mu S, g_{dsX} \approx 125nS.$$

- Now back to the assumption that we made that $W = 10\mu m$. This is not the actual value that we will use for our design. But the good news is that I_D is always proportional to W irrespective of the operating region and the model of the MOSFET (regardless square-law is valid or no). Thus, we can use ratio and proportion (cross-multiplication) to determine the correct width at which the current will be $I_{DQ} = 10\mu A$ as given in the specs. Calculate W as shown below.

$W = 10\mu m$	$W_{actual} = ??$
$I_D = 5\mu A$	$I_D = 10\mu A$

$$W_{actual} \approx 20\mu m.$$

- Now we are almost done with the design of the amplifier. Note that g_m is also proportional to W as long as V_{ov} is constant. On the other hand, $r_o = 1/g_{ds}$ is inversely proportional to $W(I_D)$ as long as L is constant. Before leaving this part, calculate g_{mQ} and g_{dsQ} using ratio and proportion (cross-multiplication).

$W = 10\mu m$	$W = 20\mu m$
$g_m = 50\mu S$	$g_{mQ} = ??$

$$g_{mQ} \approx 100\mu S.$$

$W = 10\mu m$	$W = 20\mu m$
$g_{ds} = 125nS$	$g_{dsQ} = ??$


$$g_{dsQ} \approx 250nS.$$

Part 2: CD Amplifier

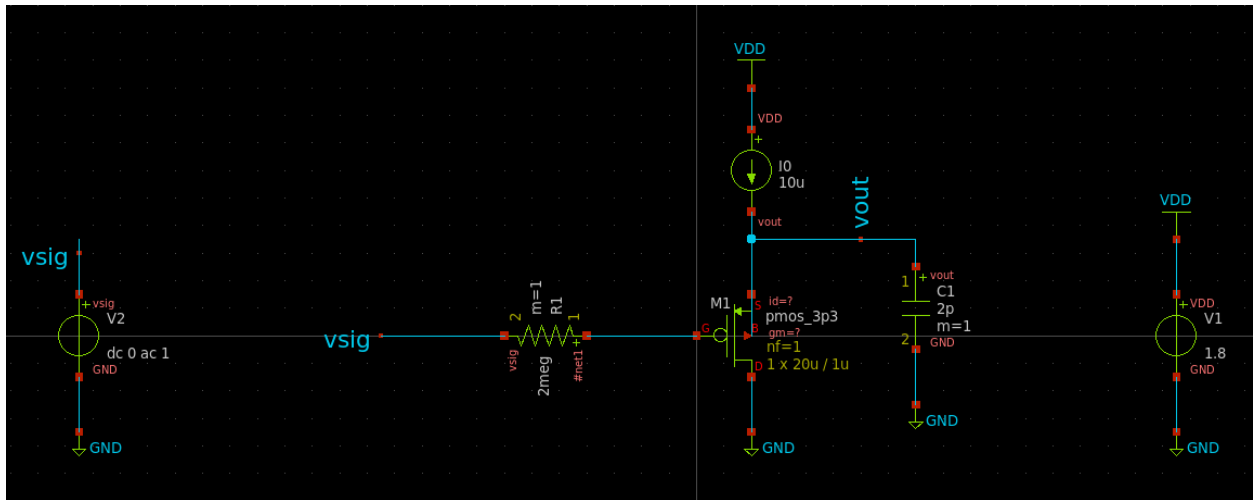1. OP (Operating Point) Analysis

- Create a new schematic for the CD amplifier (the schematic is not included in the lab document and is left for the student as an exercise). Use a PMOS and use a $10\mu A$ ideal current source for biasing (note that the current source will be connected to the source terminal). Connect the source to the bulk. Use $L = 1\mu m$ and W as determined in Part 1. Use $C_L = 2pF, R_{sig} = 2M\Omega$, (in

xschem resistor, use “value =2 meg”, and a DC input voltage = 0V.



Required schematic

- Simulate the OP point. Report a snapshot clearly showing the following parameters using the following code (in another “code_shown” dedicated for simulations only).

```
device      m.xml1.m0
model      pmos_3p3.13
gm          0.000101952
gds         2.30032e-07
id          1e-05
vgs         0.939892
vth         0.784486
vds         0.939892
vdsat       0.152948
gmbs        4.81794e-05
cdb         -9.96716e-15
cgd         -1.42526e-17
cgs         -5.11101e-14
csb         -1.49263e-14
```

Required parameters

```
ID=      gm=      gds=      vgs=      vth=      vds=      vdsat=
1e-05    0.000102    2.304e-07    0.9383    0.7829    0.9383    0.1529
```


Parameter annotation

- Check that the transistor operates in saturation.

V_{DS}	V_{Dsat}	Sat??
0.93V	0.15V	Yes

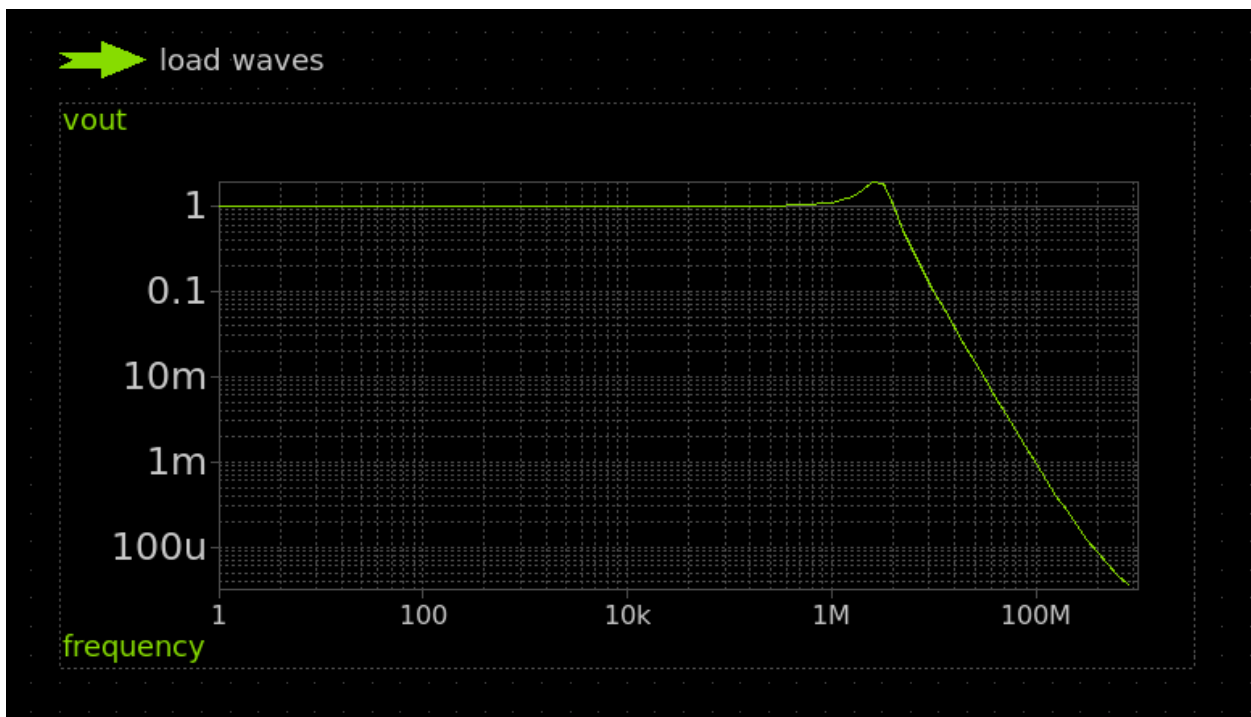2. AC Analysis

- Create a new simulation configuration and run AC analysis (from 1Hz to 1GHz) (For ignoring previous code, add ** in the beginning of each line. Always let .control and .endc) Report Bode plot magnitude in dB vs frequency.




Bode mag plot

- Do you notice frequency domain peaking?
 - The peaking in frequency domain is noticeable.
- Analytically calculate quality factor (use approximate expressions). Is the system underdamped or overdamped?

$$Q = \sqrt{\frac{g_m(C_{gs} + C_{gd})R_{sig}}{C_L}} \approx 2.6 > 0.5$$

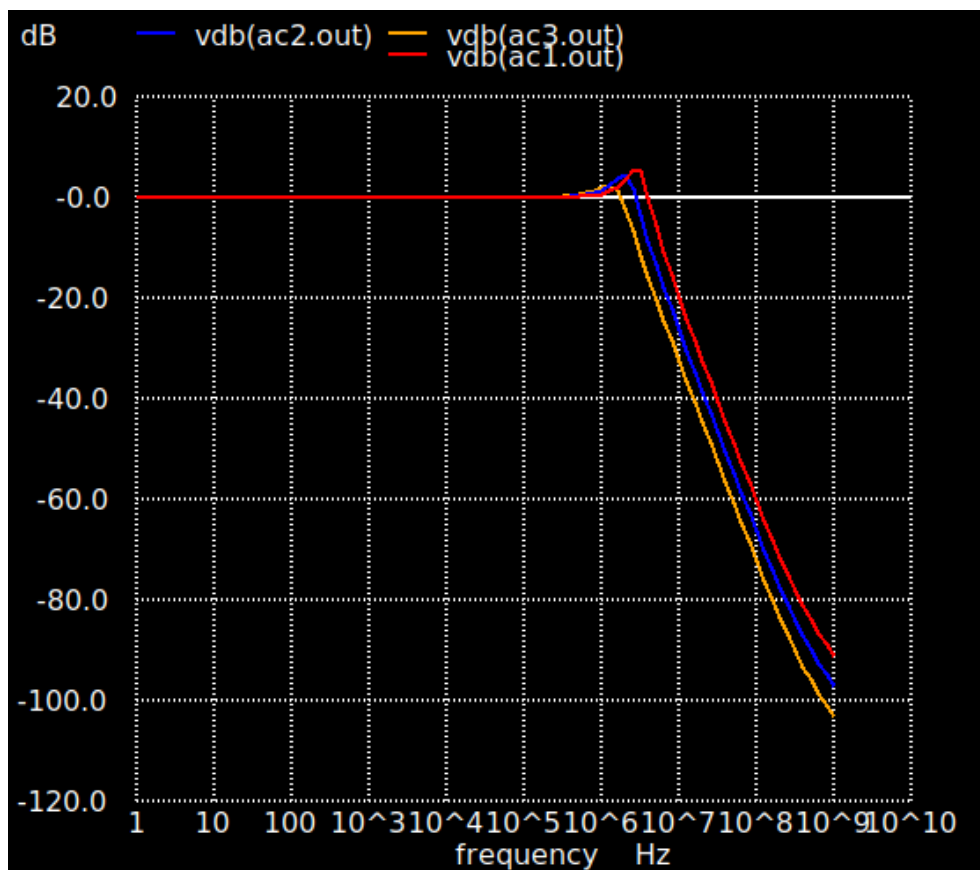- The system is underdamped.
- (Optional) Perform parametric sweep: $C_L = 2\text{p}, 4\text{p}, 8\text{p}$.
 - Report Bode plot magnitude overlaid on same plot.
 - Report the peaking vs C_L .
 - Comment.



Bode mag plot

```

No. of Data Rows : 91
peak1              = 5.526950e+00 at= 2.511886e+06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000


No. of Data Rows : 91
peak1              = 4.443462e+00 at= 1.995262e+06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 91
peak1              = 2.516250e+00 at= 1.258925e+06
binary raw file "lab4_ac_parametric.raw"
ngspice 1 -> █

```

Peaking vs CL

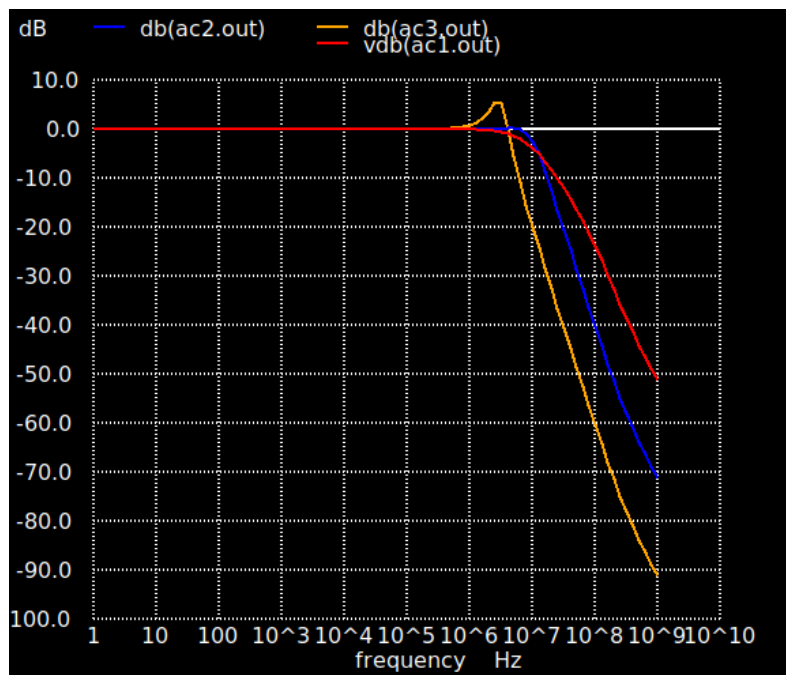- Comment: as C_L increases, Q decreases and so does the peak.
- (Optional) Perform parametric sweep: Rsig = 20k, 200k, 2M.
 - Report Bode plot magnitude overlaid on same plot.
 - Report the peaking vs Rsig.
 - Comment.



Bode mag plot

```

No. of Data Rows : 91
peak1              = -1.957876e-02 at= 1.000000e+00
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 91
peak1              = 1.725993e-01 at= 3.981072e+06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 91
peak1              = 5.527842e+00 at= 2.511886e+06
binary raw file "lab4_ac_parametric.raw"
ngspice 1 -> █

```

Peaking vs R_{sig}

- Comment: as R_{sig} increases, Q increases and so does the peak.

3. Transient Analysis


- Use a pulse source as your transient stimulus and set it as follows (delay = 2us, initial = 0V, period = 8us, pulse_value = 100mV, t_fall = 1ns, t_rise = 1ns, width = 4us). Run transient analysis for 10us to investigate the time domain ringing. Report Vin and Vout overlaid vs time.

```

No. of Data Rows : 1028
peak1              = 1.084662e+00 at= 2.181160e-06
overshoot          = 4.606572e+00 at= 5.151160e-06


```

Required calculations

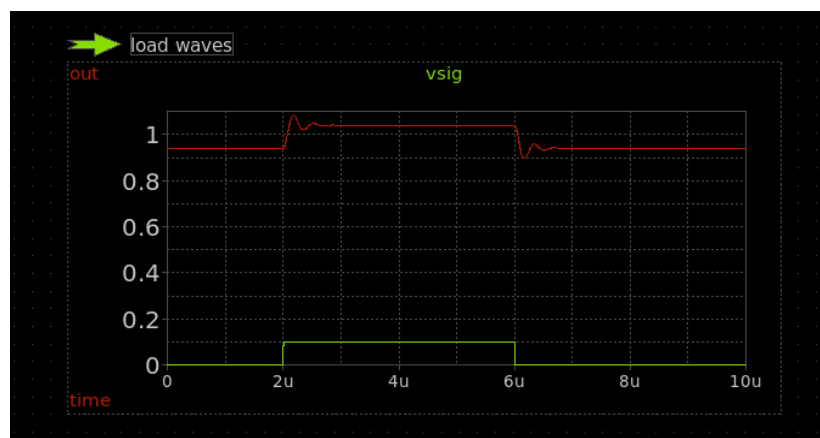

vout and vin vs time

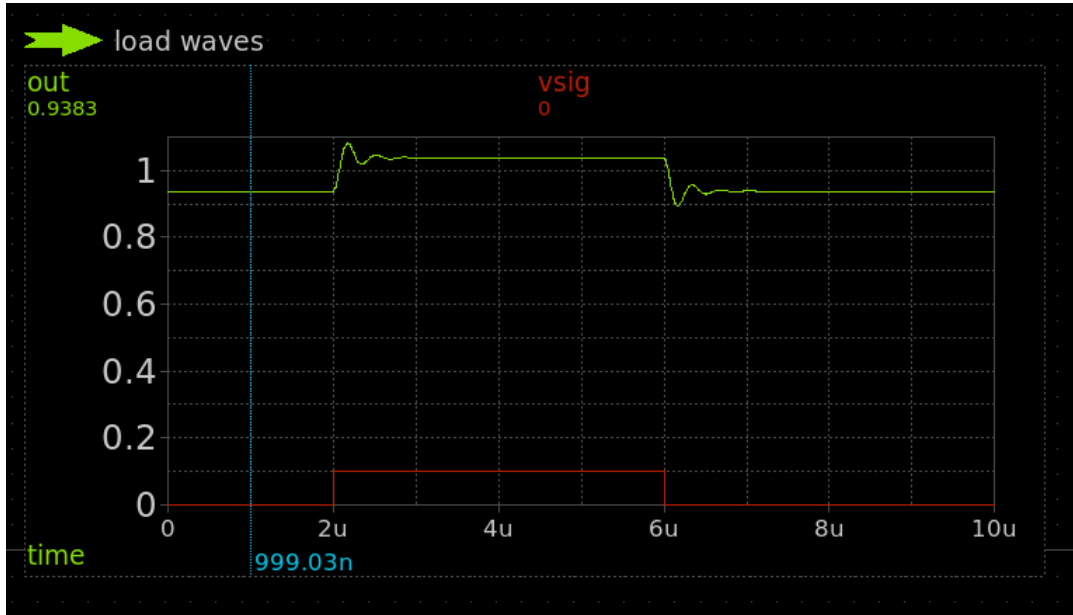- Calculate the DC voltage difference (DC shift) between V_{in} and V_{out} .
 - What is the relation between the DC shift and V_{GS} of the transistor?
 - How to shift the signal down instead of shifting it up?




DC voltage difference between v_{in} and v_{out}

- The DC shift between the i/p and the o/p is exactly the same as V_{GS} .
- By using NMOS.
- Do you notice time domain ringing? How much is the overshoot?
 - Time domain ringing is noticeable.

$$Overshoot = 100e^{\frac{-\pi}{\sqrt{4Q^2-1}}} \approx 54\%$$

- [Optional] Perform parametric sweep: $CL = 2p, 4p, 8p$.
 - Report V_{out} vs time overlaid on same plot.
 - Report the overshoot vs CL .

→ Comment.

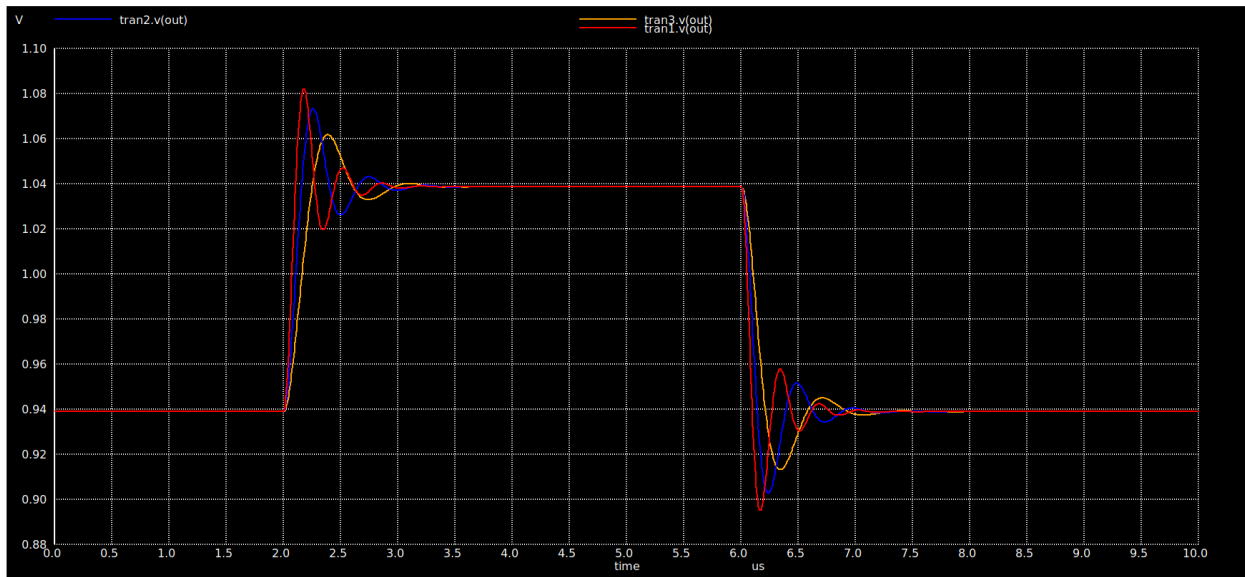

vout vs time (parametric sweep)


```
peak1          = 1.080741e+00 at= 2.181160e-06
overshoot      = 4.625822e+00 at= 5.151160e-06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
```

```
peak1          = 1.072077e+00 at= 2.261160e-06
overshoot      = 3.701559e+00 at= 5.041160e-06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
```

```
peak1          = 1.060525e+00 at= 2.381160e-06
overshoot      = 2.469233e+00 at= 5.031160e-06
binary raw file "lab4_parametric.raw"
binary raw file "/home/tare/.xschem/simulations/lab4.raw"
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
```

Overshoot vs CL

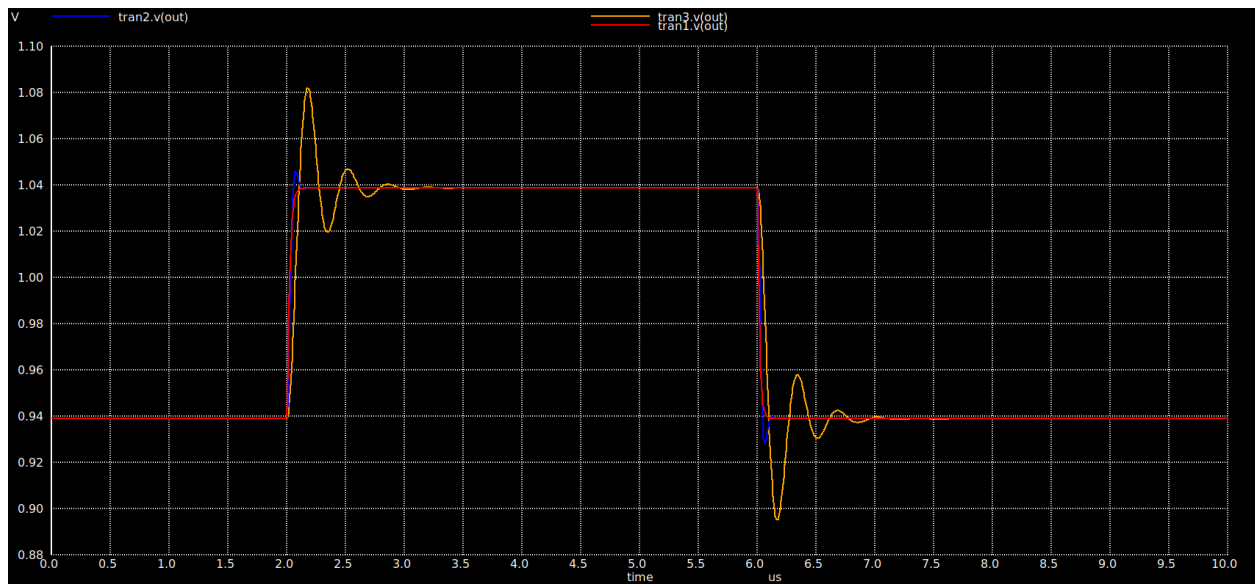- Comment: as C_L increases, Q decreases and thus the overshoot is suppressed more and more.
- [Optional] Perform parametric sweep: $R_{sig} = 20k, 200k, 2M$.
 - Report V_{out} vs time overlaid on same plot.
 - Report the overshoot vs R_{sig} .
 - Comment.



vout vs time (parametric sweep over Rsig)

```
peak1          = 1.038241e+00 at= 3.235523e-06
overshoot      = 1.091740e-04 at= 5.675523e-06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
```

```
peak1          = 1.045456e+00 at= 2.071160e-06
overshoot      = 7.691022e-01 at= 5.241160e-06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
```

```
peak1          = 1.081602e+00 at= 2.181160e-06
overshoot      = 4.621636e+00 at= 5.151160e-06
binary raw file "lab4_parametric.raw"
receive 1 -\
```


Overshoot vs Rsig

- Comment: As R_{sig} increases, Q increases and so does the overshoot.

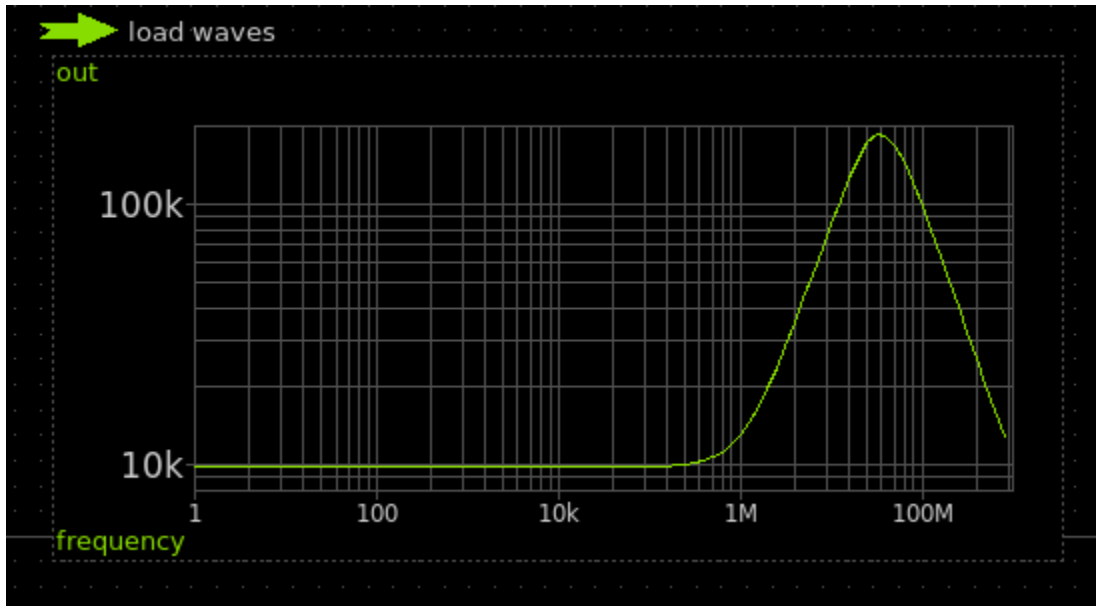
4. [Optional] Z_{out} (Inductive Rise)

- We want to simulate the CD amplifier output impedance. Replace CL with an current source (isource) with ac magnitude = 1. Remove the AC input signal. Perform AC analysis (1Hz:10GHz, logarithmic, 10points/decade). The voltage across

the AC current source is itself the output impedance. Plot the output impedance (magnitude and phase) vs frequency. Do you notice an inductive rise? Why?



Z_{out} vs frequency

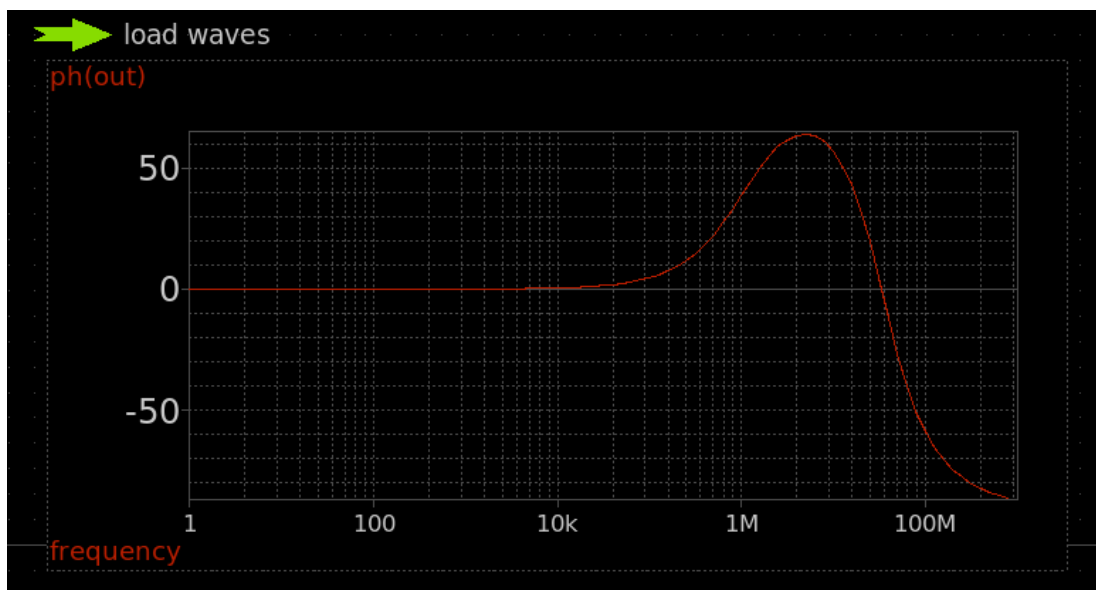

$\phi(Z_{out})$ vs frequency

- The inductive rise is noticeable, since there is a zero formed by C_{gs} and R_{sig} .

- Does Z_{out} fall at high frequency? Why?
 - Z_{out} falls at high frequency due to the dominance of the pole formed by R_{sig} and C_{gd} .