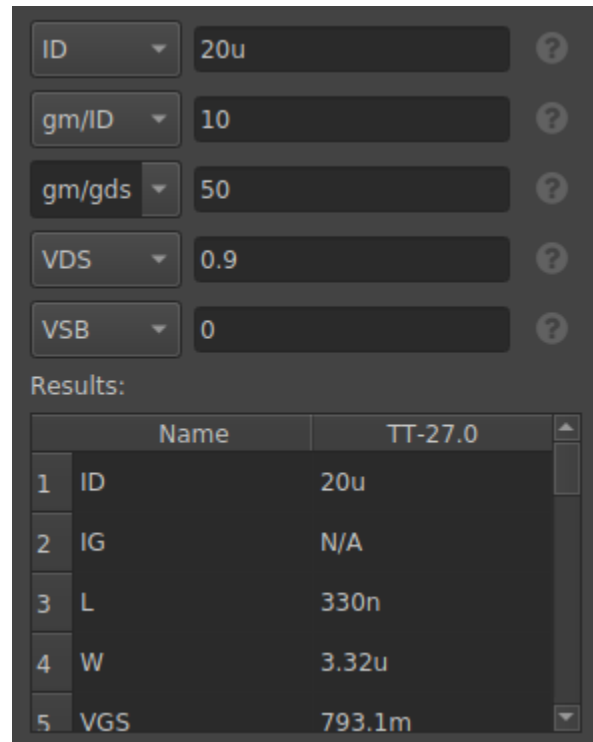


CMOS AIC design - ITI - Lab 3

Part 1: Device Sizing using ADT SA

- Take the values of L , W and V_{GS0} to xschem




Name		TT-27.0
1	ID	20u
2	IG	N/A
3	L	330n
4	W	3.32u
5	VGS	793.1m

Values of W , L and V_{GS0}

PART 2: Cascode for Gain

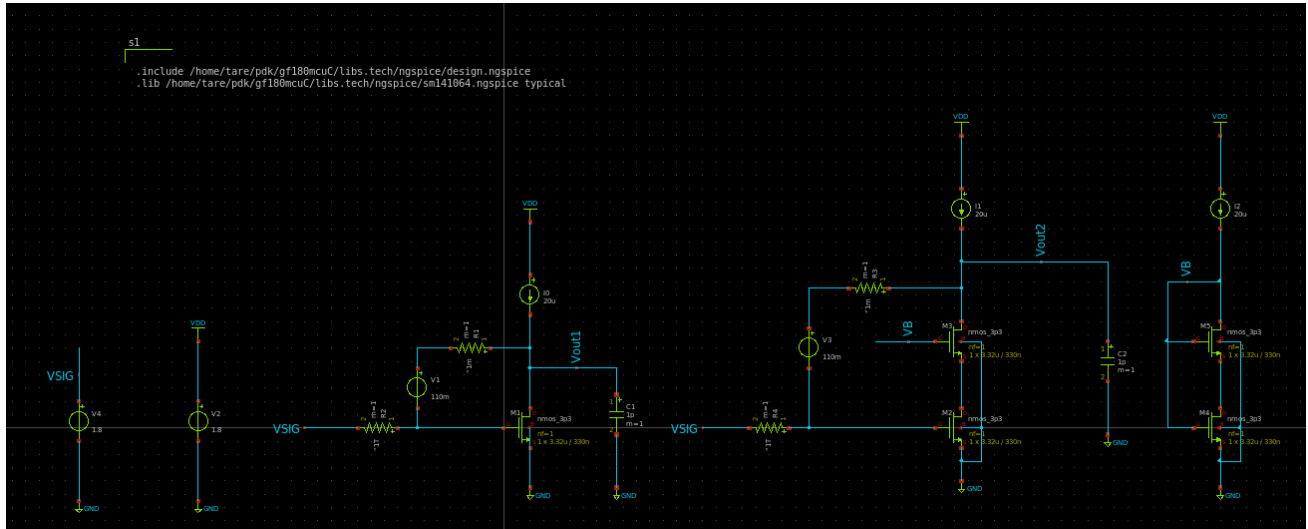1. OP Analysis

- Create a new schematic. Construct the circuit shown below. Use $I_B = 20\mu A$. Use L and W as selected in Part 1 for M_0 , M_1 , M_2 , and M_4 . Use the same W for M_3 but it will have different L as will be shown later. Use $C_L = 1pF$.



Required circuit


$$- X = V_{DS} - V_{GS} = 0.9 - 790m = 110mV.$$

ID	20u	?
W	3.32u	?
L	330n	?
VDS	0.45	?
VSB	0	?
Results:		
	Name	TT-27.0
4	W	3.32u
5	VGS	804m

ID	20u	?
W	3.32u	?
L	330n	?
VDS	0.45	?
VSB	0.45	?
Results:		
	Name	TT-27.0
4	W	3.32u
5	VGS	909.8m

VGS1 (left) and VGS2 (right)
 
$$- V_B = V_{GS2} + V_{DS1} = 910 + 450 = 1.36V.$$



$L_3 = 4.8 \mu\text{m}$

- Simulate the DC OP point of the above CS and cascode amplifiers (ngspice interactive). Report a snapshot showing the following parameters for M0 to M4 in addition to DC node voltages clearly annotated.


```

igain0 = 4.709365e+01
igain1 = 1.472122e+03
binary raw file "lab3.raw"
BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm3.m0      m.xm4.m0      m.xm2.m0
  model        nmos_3p3.10    nmos_3p3.8    nmos_3p3.8
  id           2e-05         2e-05         2e-05
  vgs          1.36188       0.89429       0.918428
  vds          0.467575      0.894283      0.471727
  vth          0.655211      0.765221      0.783969
  vdsat        0.548127      0.164367      0.167981
  gm           4.64087e-05    0.000198544   0.000195551
  gds          1.17144e-05    4.56889e-06   5.66809e-06
  gmbs         1.79444e-05    4.08522e-05   4.10553e-05
  cdb          -8.10978e-15    -1.98582e-16   -2.0581e-16
  cgd          -4.1443e-15    2.53688e-17   2.08393e-17
  cgs          -4.50086e-14    -2.36991e-15   -2.3946e-15
  csb          -1.07759e-14    -2.97466e-16   -3.06532e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm1.m0      m.xm0.m0
  model        nmos_3p3.8    nmos_3p3.8
  id           2e-05         2e-05
  vgs          0.805187      0.788612
  vds          0.443437      0.898604
  vth          0.672999      0.662321
  vdsat        0.164615      0.160693
  gm           0.000196005    0.000199136
  gds          5.55792e-06    4.22852e-06
  gmbs         5.35504e-05    5.40463e-05
  cdb          -2.67679e-16    -2.61351e-16
  cgd          1.40214e-17    1.94042e-17
  cgs          -2.34111e-15    -2.31112e-15
  csb          -3.98209e-16    -3.91504e-16

```

DC OP simulation results

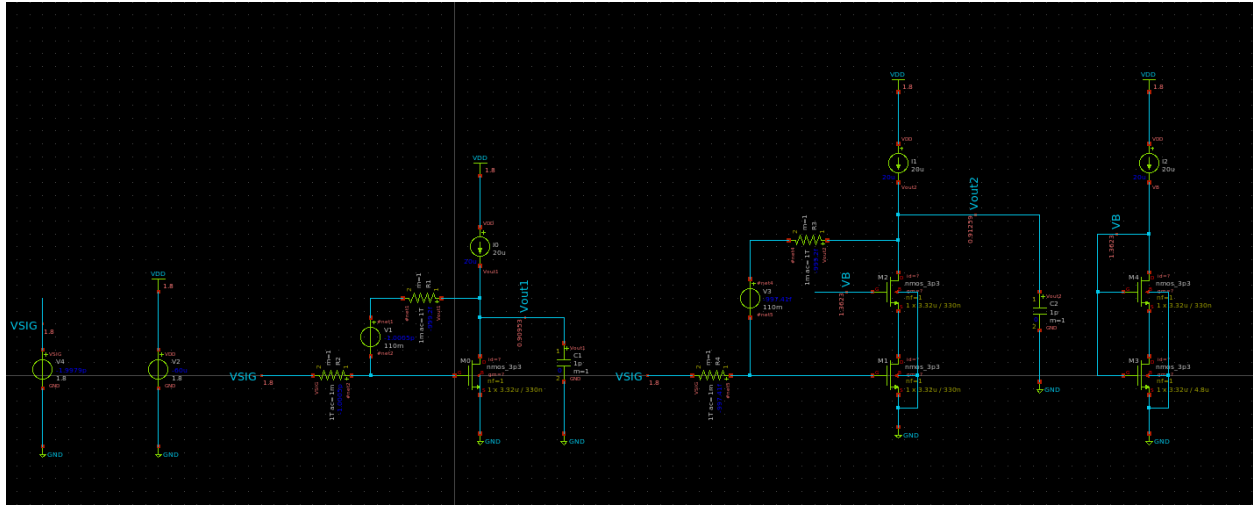

Annotated DC node voltages

- Put the OP of all transistors in a table with the appropriate units.

#	I_D	V_{GS}	V_{DS}	V_{th}	V_{Dsat}	g_m
0	20uA	0.8V	0.9V	0.7V	0.16V	200uS
1	20uA	0.9V	0.44V	0.67V	0.16V	196uS
2	20uA	0.9V	0.47V	0.78V	0.16V	195uS
3	20uA	1.36V	0.46V	0.66V	0.55V	46uS
4	20uA	0.9V	0.46V	0.77V	0.16V	200uS

#	g_{ds}	g_{mb}	C_{db}	C_{gd}	C_{gs}	C_{sb}
0	4.2uS	54uS	$2.6e - 16F$	$2e - 17F$	$2.3e - 15F$	$4e - 16F$
1	5.6uS	54uS	$2.7e - 16F$	$1.4e - 17F$	$2.4e - 15F$	$4e - 16F$
2	5.7uS	41uS	$2e - 16F$	$2.9e - 17F$	$2.4e - 15F$	$3e - 16F$
3	12uS	18uS	$8e - 15F$	$4.2e - 15F$	$4.5e - 14F$	$1e - 14F$
4	4.6uS	40uS	$2e - 16F$	$2.5e - 17F$	$2.4e - 15F$	$3e - 16F$

- Check that all transistors operate in saturation. Does any transistor operate in triode? Why?

#	V_{DS}	$V_{DS,sat}$	<i>OP Region</i>
0	0.9	0.16	<i>Sat</i>
1	0.45	0.16	<i>Sat</i>
2	0.46	0.16	<i>Sat</i>
3	0.46	0.55	<i>Triode</i>
4	0.9	0.16	<i>Sat</i>

- M3 is operating in triode, since it has $V_{OV} = V_B - V_{th} = 1.36 - 0.66 = 0.7V$, which is higher than $V_{DS} = 0.44V$.
- Do all transistors have the same v_{th} ? Why?
 - The CS transistor and the i/p transistor of the cascode have the same V_{th} as the source-body voltage for both devices is zero and thus no body effect, while the cascode transistor has non-zero V_{SB} and therefore the threshold is slightly higher.
- What is the relation ($\ll, <, \approx, >, \gg$) between g_m and g_{ds} ?

$$g_m \gg g_{ds}$$

- What is the relation ($\ll, <, \approx, >, \gg$) between g_m and g_{mb} ?

$$g_m > g_{mb}$$

- What is the relation ($\ll, <, \approx, >, \gg$) between c_{gs} and c_{gd} ?

$$C_{gs} > C_{gd}$$

- What is the relation ($\ll, <, \approx, >, \gg$) between c_{sb} and c_{db} ?

$$C_{sb} > C_{db}$$

2. AC Analysis


- Perform AC analysis (1Hz:10GHz, logarithmic, 10points/decade) to simulate gain and bandwidth. create expressions for circuit parameters (DC gain, BW, GBW, and UGF) and export them to interactive.

```

peak1          = 4.709049e+01 at= 1.000000e+00
f3db1          = 6.730899e+05
ugf1           = 3.159338e+07
gbw1 = 3.169613e+07
peak2          = 1.504826e+03 at= 1.000000e+00
f3db2          = 2.024958e+04
ugf2           = 3.064112e+07
gbw2 = 3.047209e+07
  
```

Required calculations

 - Report the Bode plot (magnitude) of CS and cascode appended on the same plot.



Bode mag plot

- Using small signal parameters from OP simulation or SA, perform hand analysis to calculate DC gain, BW, and GBW of both circuits.

DC gain

$$CS: A_v = g_m r_o = 200\mu \times (4\mu)^{-1} = 50$$

$$Casc: A_v = g_{m,i/p} r_{o,casc} (g_{m,casc} + g_{mb,casc}) r_{o,i/p} \\ = 195\mu (5.6\mu)^{-1} (195\mu + 40\mu) (4.2\mu)^{-1} \approx 1950$$

BW

$$CS: BW = \frac{1}{2\pi R_o C_o} = \frac{4.2\mu}{2\pi (2.6e-16 + 1.9e-17(1 + \frac{1}{47}) + 1p)} = 668k$$

$$Casc: BW = \frac{1}{2\pi R_o C_o} = \frac{1}{2\pi ((5.6\mu)^{-1} (195\mu + 40\mu) (4.2\mu)^{-1}) (2e-16 + 2e-17 + 1p)} \\ \approx 19k$$

<i>GBW</i>
<i>CS: $GBW = 50 \times 668k = 33.4M$</i>
<i>Casc: $GBW = 1950 \times 19k = 37M$</i>

- Report a table comparing the DC gain, BW, UGF, and GBW of both circuits from simulation and hand analysis.

<i>CS</i>		
<i>Parameter</i>	<i>Simulated</i>	<i>Calculated</i>
<i>DC gain</i>	47	50
<i>BW</i>	670k	668k
<i>GBW</i>	31.5M	33.4M


<i>Casc</i>		
<i>Parameter</i>	<i>Simulated</i>	<i>Calculated</i>
<i>DC gain</i>	1.5k	1950
<i>BW</i>	20k	19k
<i>GBW</i>	30M	37M

- Comment: It can be easily noticed that the cascode stage provides much larger gain than the CS stage, but has a lower bandwidth.

Part 3: Cascode for BW

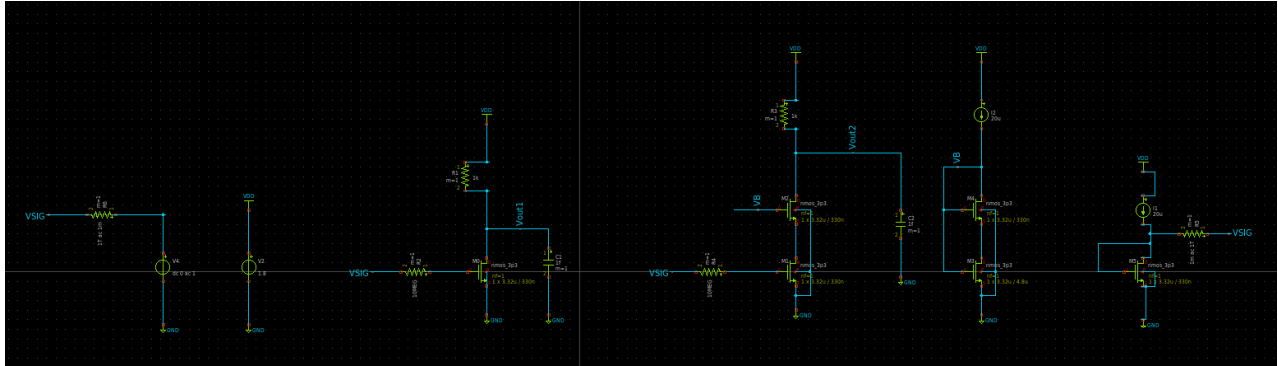1. OP Analysis

- Create a new schematic. Copy the old schematic instances to the new one. Make the following modifications: xxx



Required circuit

- Calculate R_D analytically such that the voltage drop on it is $\approx V_{DD}/2$ (the current remains roughly the same as in Part 2 because we are using the VGS generated by M5). Note that the DC voltage of the output node is set by the resistance (R_D); thus, we don't need a feedback loop as in the previous case.

$$R_D = \frac{V_{DD}/2}{I_D} = \frac{0.9}{20\mu} = 45k\Omega.$$

- Simulate the DC OP point of the new CS and cascode amplifiers. Report a snapshot showing the following parameters for M0 to M5 in addition to DC node voltages clearly annotated.


```

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.xm3.m0      m.xm5.m0      m.xm4.m0
model       nmos_3p3.10  nmos_3p3.8    nmos_3p3.8
id          2e-05       2e-05         2e-05
vgs         1.36484     0.796226      0.910802
vds         0.454022    0.796219      0.910794
vth         0.654459    0.668728      0.781517
vdsat       0.550918    0.161512      0.164557
gm          4.50895e-05  0.000198656   0.000198257
gds         1.3775e-05   4.3479e-06    4.53717e-06
gmbs        1.75277e-05  5.39979e-05   4.10728e-05
cdb         -8.29324e-15     -2.62373e-16  -1.99924e-16
cgd         -4.8947e-15    1.91849e-17   2.52409e-17
cgs         -4.48635e-14    -2.31708e-15  -2.36946e-15
csb         -1.08404e-14    -3.92855e-16  -2.99493e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.xm2.m0      m.xm1.m0      m.xm0.m0
model       nmos_3p3.8    nmos_3p3.8    nmos_3p3.8
id          1.86315e-05  1.86315e-05   2.00566e-05
vgs         0.914593    0.796227      0.796226
vds         0.51132     0.450233      0.89744
vth         0.78776     0.671309      0.669481
vdsat       0.162861    0.159772      0.161026
gm          0.00018822    0.000188475   0.000199326
gds         5.15076e-06   5.19531e-06   4.23567e-06
gmbs        3.93478e-05     5.14664e-05   5.4105e-05
cdb         -2.02467e-16          -2.64884e-16  -2.61519e-16
cgd         2.20772e-17          1.44378e-17   1.94153e-17
cgs         -2.36636e-15          -2.3139e-15   -2.31281e-15
csb         -3.02023e-16          -3.94284e-16  -3.91752e-16

```

Required parameters

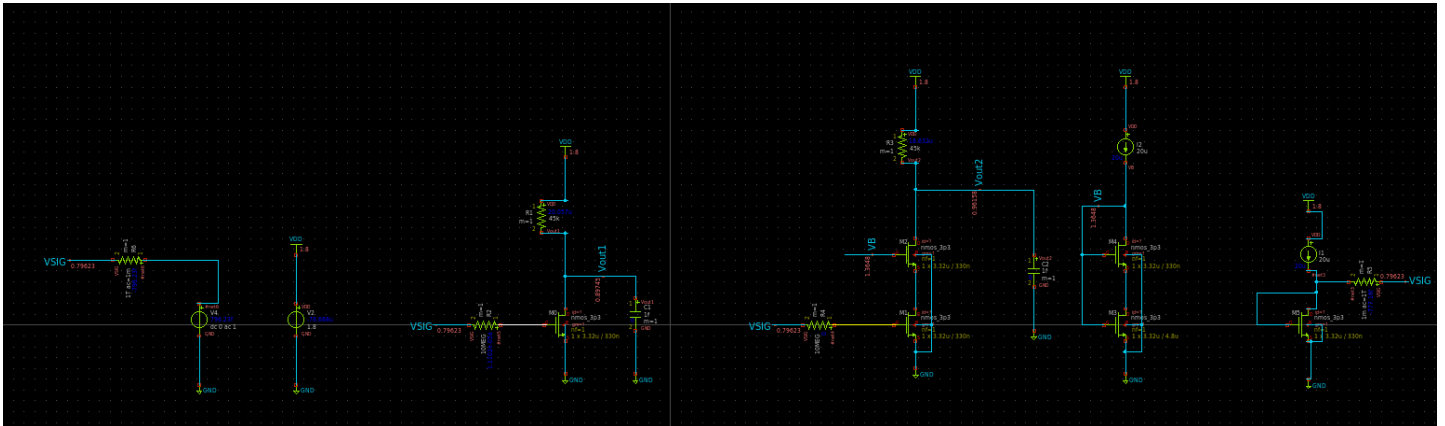

DC node voltages annotated

- Check that all transistors operate in saturation. Does any transistor operate in triode? Why?

#	V_{DS}	$V_{DS,sat}$	<i>OP Region</i>
0	0.9	0.16	<i>Sat</i>
1	0.45	0.16	<i>Sat</i>
2	0.5	0.16	<i>Sat</i>
3	0.45	0.55	<i>Triode</i>
4	0.9	0.16	<i>Sat</i>
5	0.8	0.16	<i>Sat</i>

- M3 is operating in triode, since it has $V_{OV} = V_B - V_{th} = 1.36 - 0.66 = 0.7V$, which is higher than $V_{DS} = 0.45V$.

2. AC Analysis

- Perform AC analysis (1Hz:10GHz, logarithmic, 10points/decade) to simulate gain and bandwidth. Use calculator to create expressions for circuit parameters (DC gain, BW, GBW, and UGF) and export them.


```

No. of Data Rows : 101
peak1              = 7.639994e+00 at= 1.000000e+00
f3db1              = 1.833668e+06
ugf1               = 1.402092e+07
gbw1 = 1.400921e+07
peak2              = 8.892122e+00 at= 1.000000e+00
f3db2              = 3.210282e+06
ugf2               = 2.866316e+07
gbw2 = 2.854622e+07

```

Required calculations

 - Report the Bode plot (magnitude) of CS and cascode appended on the same plot.



Bode mag plot

- Using small signal parameters from OP simulation or SA, perform hand analysis to calculate DC gain, BW, and GBW of both circuits.

DC gain

$$CS: A_v \approx g_m R_D = 190\mu \times 45k = 8.6$$

$$Casc: A_v \approx g_{m,i/p} R_D = 190\mu \times 45k \approx 8.6$$

BW

$$CS: BW = \frac{1}{2\pi R_i C_i} = \frac{1}{2\pi(10M)(2.8e-15 + 540e-18(1+8.6) + 607e-18)} = 1.97M$$

*Values from ADT **

$$Casc: BW = \frac{1}{2\pi R_o C_o} = \frac{1}{2\pi(10M)(3f+640a(1+1)+640a)} \approx 3.5M$$

*Values from ADT **

GBW

$$CS: GBW = 8.6 \times 1.97M = 17M$$

$$Casc: GBW = 8.6 \times 3.5M = 30.1M$$

- Report a table comparing the DC gain, BW, UGF, and GBW of both circuits from simulation and hand analysis. Comment on the results.

CS

<i>Parameter</i>	<i>Simulated</i>	<i>Calculated</i>
<i>DC gain</i>	7.6	8.6
<i>BW</i>	1.8M	1.97M
<i>GBW</i>	14M	17M

Casc

<i>Parameter</i>	<i>Simulated</i>	<i>Calculated</i>
<i>DC gain</i>	8.9	8.6
<i>BW</i>	3.2M	3.5M
<i>GBW</i>	29M	30.1M

- Comment: It can be noticed that the cascode stage provides almost the same gain as the CS stage due to the

severe reduction of o/p impedance, but has more bandwidth (around 2 times the BW of CS).