

# CMOS AIC design - ITI - Lab 2

## Part 1: Sizing Charts


- Assuming CM output =  $V_{R_D} = V_{DD}/2$  and given the DC bias current, determine the value of  $R_D$ .

$$R_D = \frac{V_{R_D}}{I_D} = \frac{0.9}{100\mu} = 9k\Omega.$$

- Given  $A_v$  and  $V_{R_D}$ , calculate the required  $V^*$  (again note that  $V^* \neq V_{OV}$  for a real MOSFET). Let's name this value  $V_Q^*$ .

$$V_Q^* = \frac{2V_{R_D}}{|A_v|} = \frac{1.8}{8} = 225mV.$$

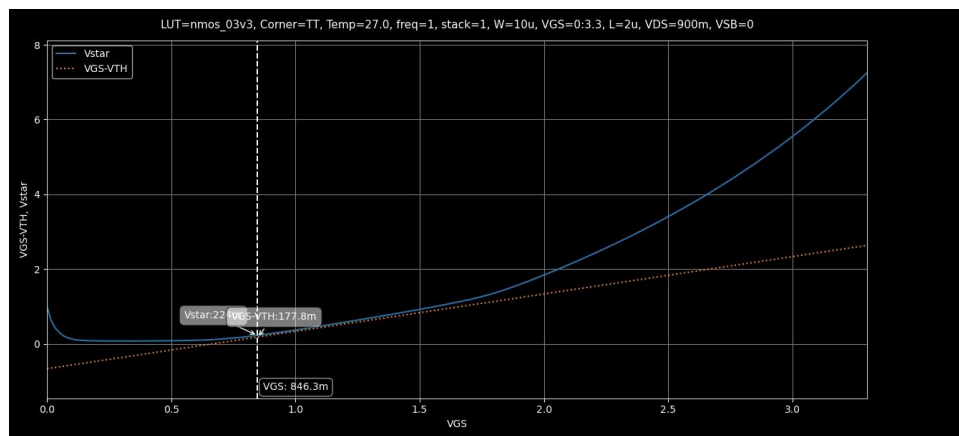
- On the  $V^*$  and  $V_{OV}$  chart locate the point at which  $V^* = V_Q^*$ . Find the corresponding  $V_{OVQ}$  and  $V_{GSQ}$ .



$V^*$  and  $V_{ov}$  VS  $V_{GS}$

$$V_{OVQ} \approx 180mV, V_{GSQ} \approx 845mV$$

 - Plot  $I_D$ ,  $g_m$ , and  $g_{ds}$  vs  $V_{GS}$ . Find their values at  $V_{GSQ}$ . Let's name these values  $I_{DX}$ ,  $g_{mX}$ , and  $g_{dsX}$ .



$I_D$ ,  $g_m$ ,  $g_{ds}$  VS  $V_{GS}$

$$I_{DX} \approx 13uA, g_{mX} \approx 120uS, g_{dsX} \approx 250nS.$$

- Now back to the assumption that we made that  $W = 10\mu m$ . This is not the actual value that we will use for our design. But the good news is that  $I_D$  is always proportional to  $W$  irrespective of the operating region and the model of the MOSFET (regardless square-law is valid or no). Thus, we can use ratio and proportion (cross-multiplication) to determine the correct width at which the current will be  $I_{DQ} = 100\mu A$  as given in the specs. Calculate  $W$ .

$10\mu m$	$W_{actual}$
$13\mu A$	$100\mu A$

$$W_{actual} = 77\mu m.$$

- Now we are almost done with the design of the amplifier. Note that  $g_m$  is also proportional to  $W$  as long as  $V_{ov}$  is constant. On the other hand,  $r_o = 1/g_{ds}$  is inversely proportional to  $W (I_D)$  as long as  $L$  is constant. Before leaving this part, calculate  $g_{mQ}$  and  $g_{dsQ}$  using ratio and proportion (cross- multiplication) and double check that  $A_v = -g_m(R_D || r_o)$  meet the required gain spec.

$10\mu m$	$77\mu m$
$120\mu S$	$g_{mQ}$

$$g_{mQ} = 925\mu S.$$

$13\mu A$	$100\mu A$
$250nS$	$g_{dsQ}$


$$g_{dsQ} = 2\mu S.$$

$$A_v = 925u(9k \parallel (2u)^{-1}) = 8.2 \approx 8.$$

## Part 2: CS Amplifier

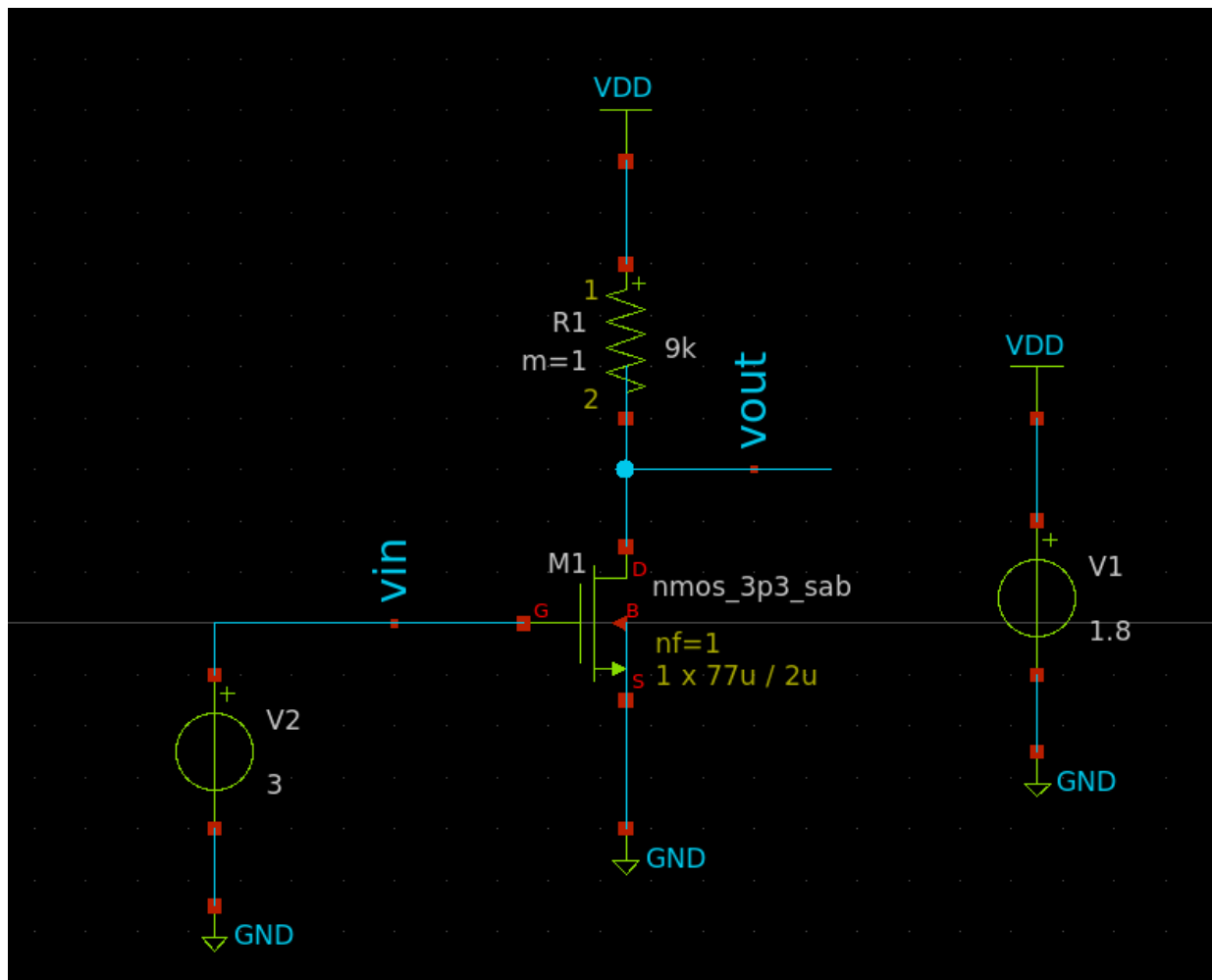
### 1. OP and AC Analysis

- Create a testbench for the resistive loaded CS amplifier using the  $V_{GSQ}$ ,  $R_D$ ,  $L$ , and  $W$  that you got from the previous part.



Required testbench

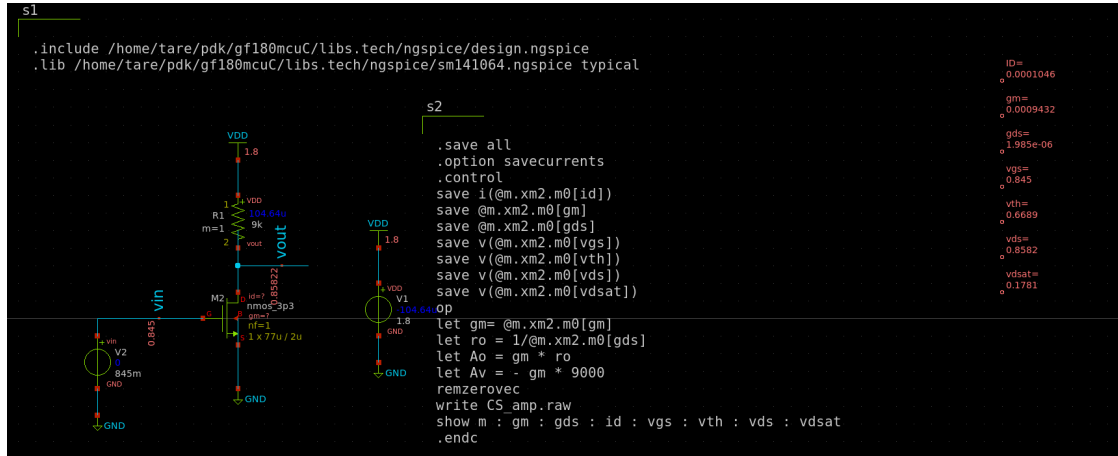- Simulate the DC OP. Report a snapshot for the key operating point (OP) parameters. Compare the results with the results you obtained in Part1.



Required snapshot

- As can be seen from the snapshot, the results from the simulation are very similar to those obtained in the previous part.
- Compare  $r_o$  and  $R_D$ . Is the assumption of ignoring  $r_o$  justified in this case? Do you expect the error to remain the same if we use min L?

$r_o$	$R_D$
$(g_{ds})^{-1} = (2u)^{-1} = 500k\Omega$	$9k\Omega$


- $r_o \gg R_D$
- Since the parallel combination is very close to  $R_D$ , ignoring  $r_o$  is justified.
- $L_{min} \rightarrow \lambda_{max} \rightarrow V_{A,min} \rightarrow r_{o,min}$ , so the error would be higher.
- Calculate the intrinsic gain of the transistor.

$$A_o = g_m r_o = 925\mu \times 500k \approx 460.$$

- Calculate the amplifier gain analytically. What is the relation ( $\ll, <, \approx, >, \gg$ ) between the amplifier gain and the intrinsic gain?

$$A_v = g_m (R_D || r_o) = 925\mu (9k || 500k) \approx 8.2.$$

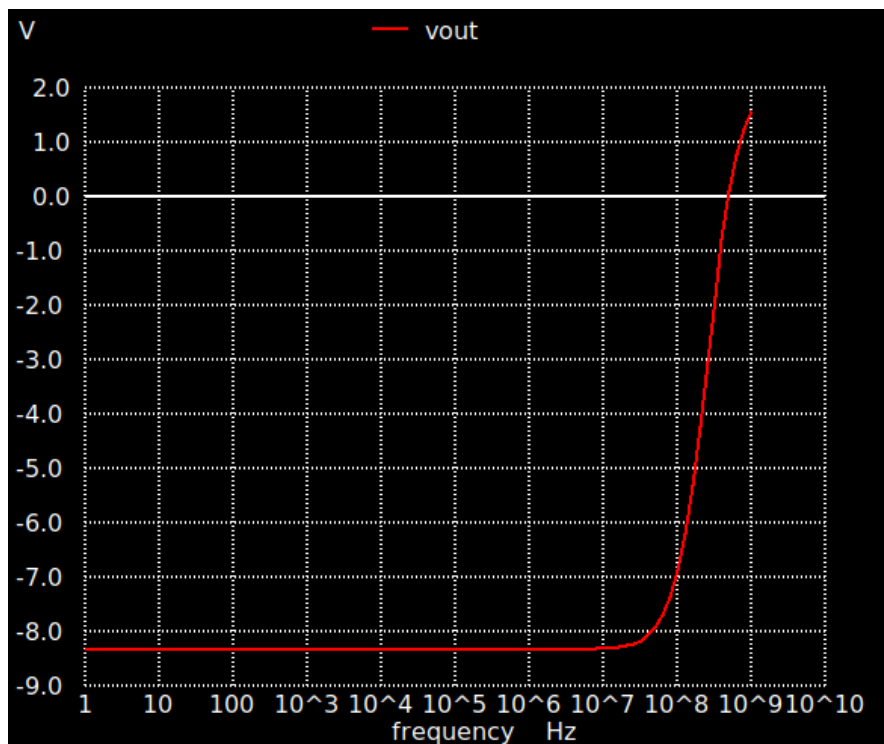- $A_o \gg A_v$ .
- Create a new simulation configuration and run AC analysis (from 1Hz to 1GHz). Report the gain vs frequency. Annotate the DC gain and make sure it meets the spec.




vout VS frequency

- As seen in the plot, DC gain  $\approx -8$  as required in specs.
 
## 2. Gain Non-linearity

- Create a new simulation configuration. Perform a DC sweep for the input voltage from 0 to  $V_{DD}$  with 2mV step. Report VOUT vs VIN. Is the relation linear? Why?




VOUT VS VIN plot

- No, the relation is not linear. At the beginning of the plot,  $V_{out}$  is constant due to the absence of drain current and thus no  $V_{DS}$  variation. This holds until  $V_{in}$  exceeds  $V_{th}$ , wherein the drain current begins to flow, inducing a voltage drop across  $R_D$  and therefore  $V_{DS}$  begins to fall in an almost linear fashion with a steep slope, then the slope begins to

be less steeper since the operating point has moved to triode region, which is characterized by small  $g_m$ 's and  $r_o$ 's (note that the slope of the curve is the gain of the circuit, which is a function of transconductance and o/p resistance).

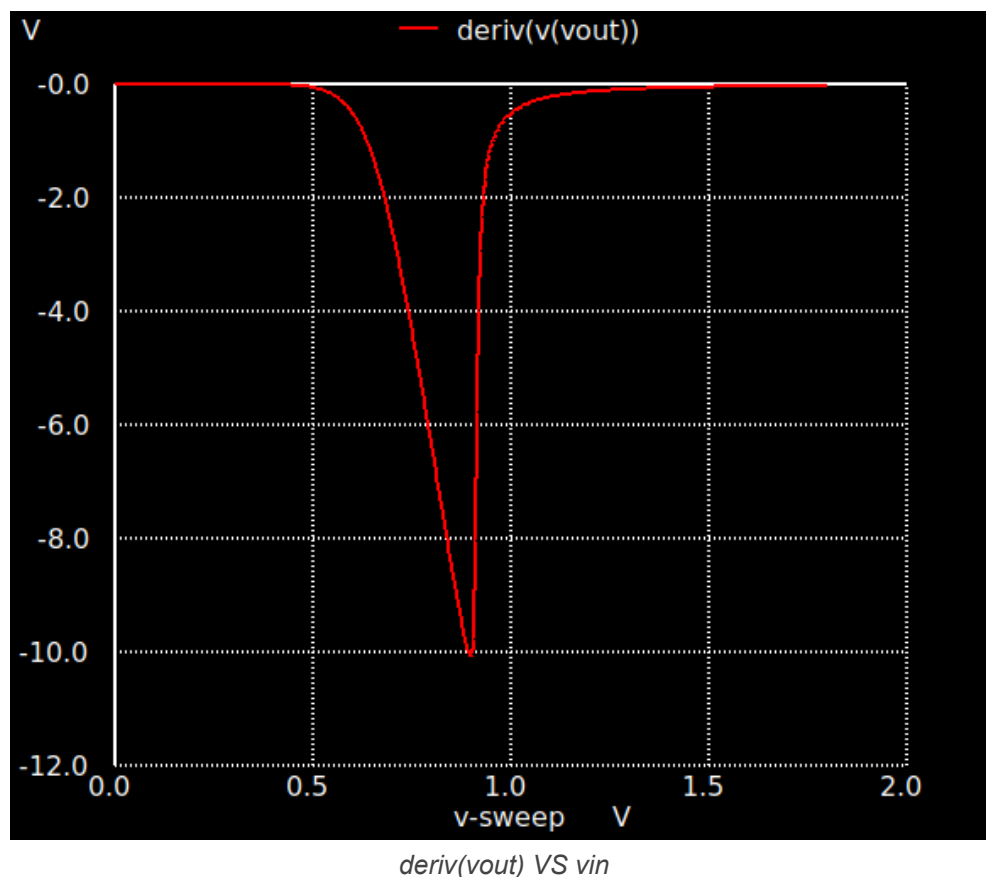
- Calculate the derivative of VOUT using calculator. Plot the derivative vs VIN. The derivative is itself the small signal gain. Is the gain linear (independent of the input)? Why?



- No, the gain depends on the i/p voltage. The gain of any CMOS amplifier is a function of  $G_m$  and  $R_o$ , which in turn are functions of the i/p voltage.
- Set the properties of the voltage source to apply a transient stimulus (sine wave of 1kHz frequency and 10mV amplitude superimposed on the DC input voltage). Create a new simulation



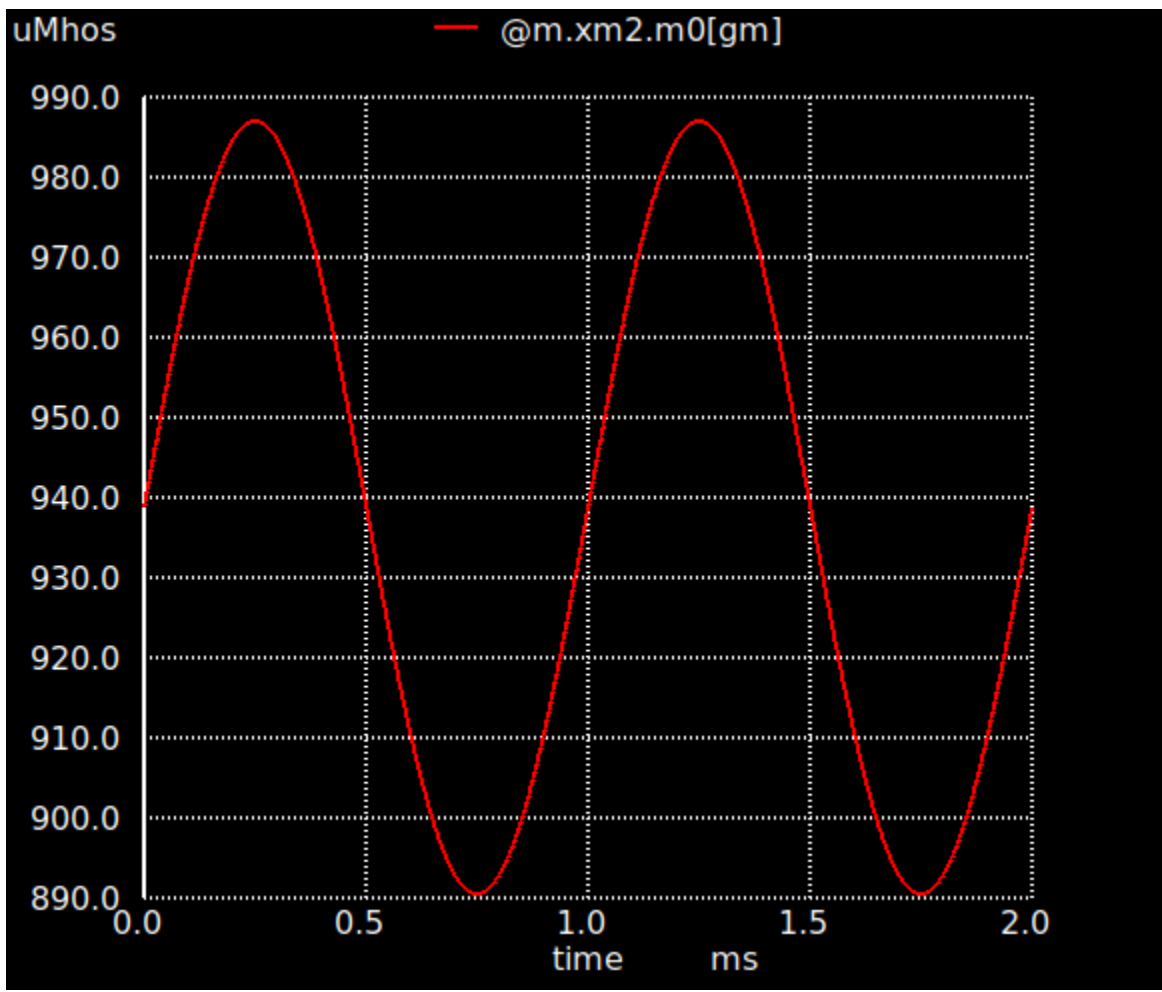configuration. Run transient simulation for 2ms. Plot gm vs time. Does gm vary with the input signal? What does that mean?



*gm VS time*

- Yes,  $g_m$  varies with the i/p signal. This means that  $g_m$  is a function of gate-source voltage, which is emphasized by the formulae of  $g_m$  derived from the square law.
- Is this amplifier linear? Comment.
  - This amplifier is *not* linear. A linear amplifier is a system that has linear transfer characteristics (i.e. a linear relation between i/p and o/p), which is not satisfied in our case, as can be easily noticed from *VOUT VS VIN* plot.