 


CMOS AIC design - ITI - Lab 7


Part 1: g_m/I_D Design Charts

Subscript index: $i \rightarrow i/p$ pair, $l \rightarrow$ load, $tcs \rightarrow$ tail current source.

- Using ADT Device Xplore, plot the following design charts vs g_m/I_D for both PMOS and NMOS. Set $V_{DS} = V_{DD}/3$ and $L = 0.33\mu, 0.4\mu, 0.4\mu, 2\mu$
 - Let $I_D = 20\mu A$. $\rightarrow g_m/g_{ds}$




 g_m / g_{ds} vs g_m / I_D @ $I_D = 20\mu A$, $V_{SB} = 0$ for NMOS




g_m / g_{ds} vs g_m / I_D @ $I_D = 20\mu A$, $V_{SB} = 0$ for PMOS

→ ID/W

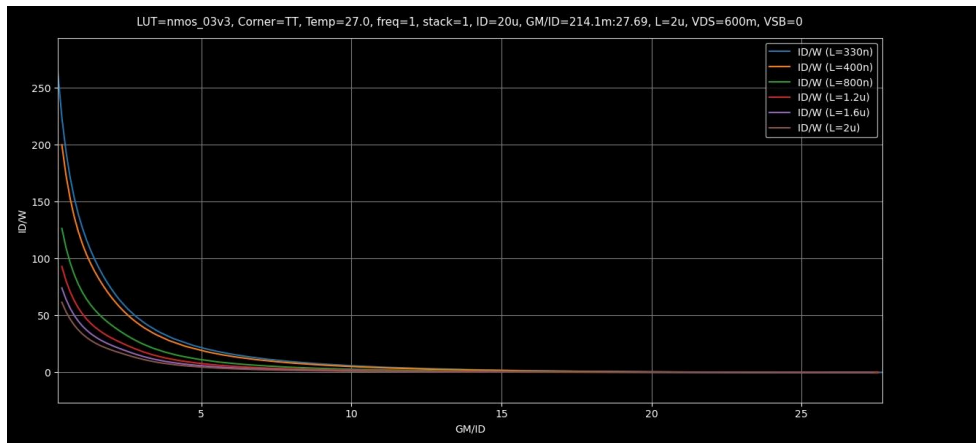


 ID / W vs gm / ID @ $ID = 20\mu A$, $V_{SB} = 0$ for **NMOS**




ID / W vs gm / ID @ $ID = 20\mu A$, $V_{SB} = 0$ for **PMOS**



→ gm/cgg

 

 gm / C_{gg} vs gm / ID @ $ID = 20\mu A$, $V_{SB} = 0$ for **NMOS**



→ VGS

 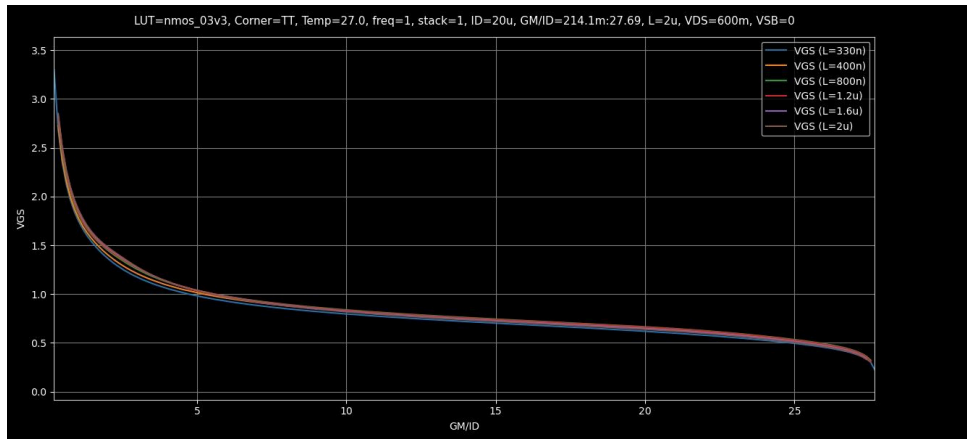

Part 2: OTA Design

- Use gm/ID methodology to design a diff input SE output operational transconductance amplifier (OTA) that achieves the following specs. Use an ideal external 10uA DC current source in your test bench (not included in the OTA current consumption spec), but design your own current mirror.

1. Design of i/p pair

- From *CMIR* spec, it can be noticed that its limits are closer to V_{DD} , thus an *NMOS* i/p pair is employed.
- From *GBW* spec: $GBW = \frac{g_{m,i}}{2\pi C_L} \Rightarrow g_{m,i} = 2\pi C_L \times GBW$.

$$g_{m,i} \approx 314\mu S.$$


- In part 1, it was assumed that $I_D = 20\mu A$. this value will be used in determining $\frac{g_m}{I_D}(i)$.

$$\frac{g_m}{I_D}(i) \approx 16S/A.$$

- $A_v = g_{m,i}(r_{o,i} || r_{o,l})$. for simplicity, let $r_{o,i} = r_{o,l} = r_{o,il}$, thus

$$A_v = \frac{g_{m,i} r_{o,il}}{2} > 43dB = 50 \Rightarrow \frac{g_{m,i}}{g_{ds,il}} > 100.$$

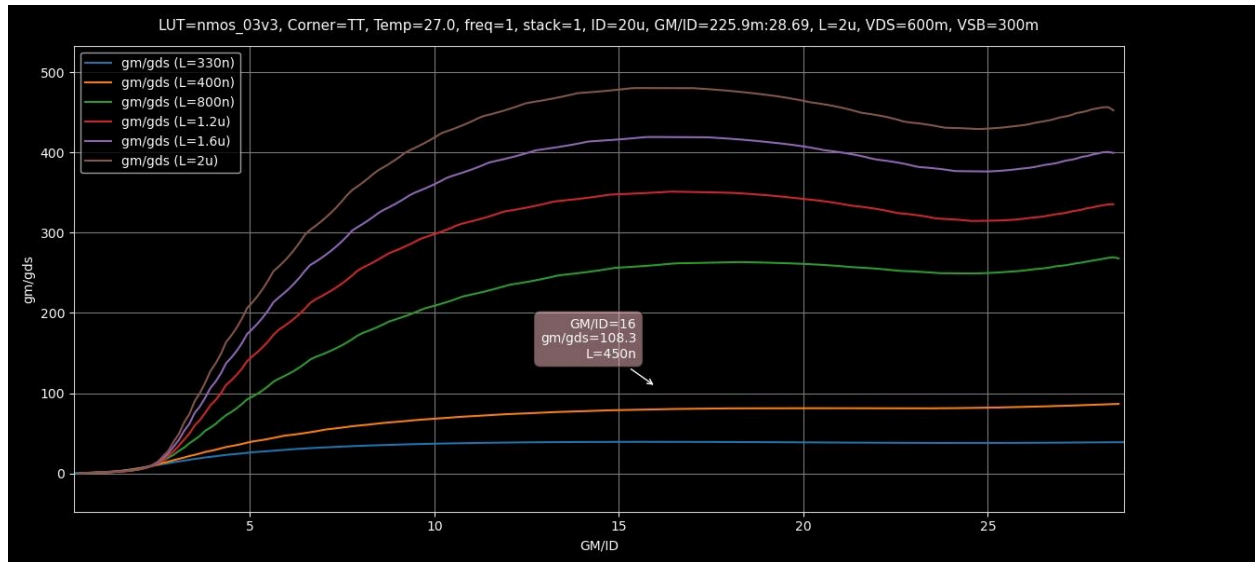
- Note that in the plots shown in part 1, body effect was not taken into consideration, so new plots, that takes the body effect into account, will be used, assuming that $V_{SB} = 0.3V$.



gm / gds for i/p pair

$$L_i = 450nm.$$

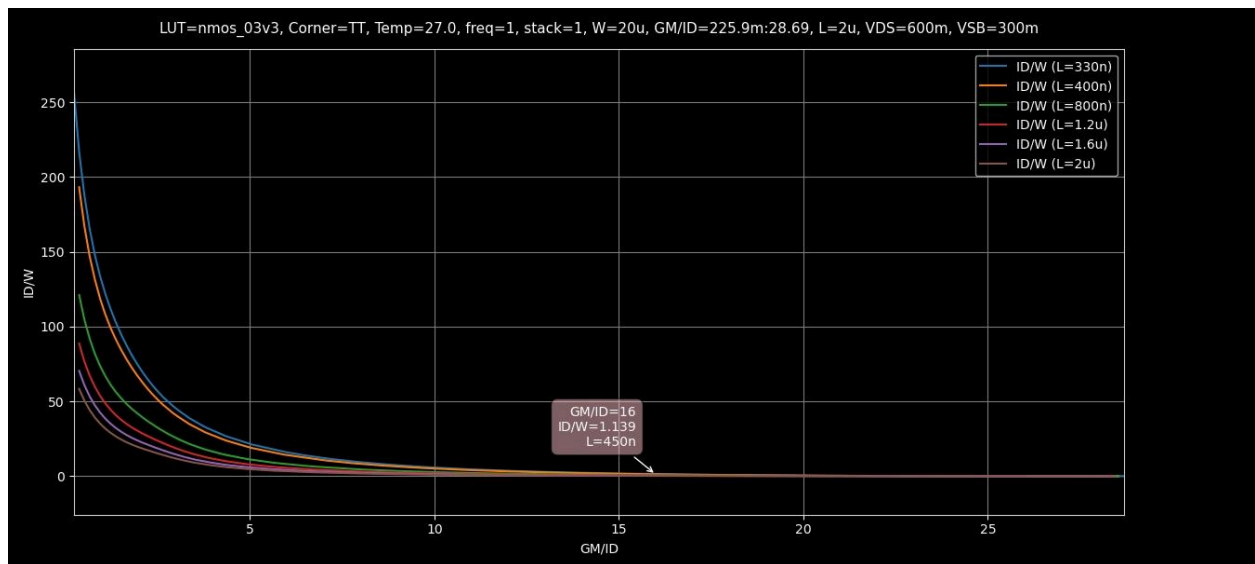- W can be selected from the current driving capability plot.



$$ID / W \approx 1.14$$

$$W_i = 20u / 1.14 = 17.5um.$$


2. Design of Load Transistors

- Let $\frac{g_m}{I_D}(l) = 15$, and given that $I_D = 20\mu A$, thus

$$g_{m,l} = 300\mu S.$$

- In the process of designing the i/p pair, it was assumed that $r_{o,i} = r_{o,l} = r_{o,il}$, also a constraint was obtained: $\frac{g_{m,i}}{g_{ds,il}} > 100$, given that $g_{m,i} \approx 314\mu S$, thus
 
$$g_{ds,il} < 3.14\mu S, \quad \frac{g_{m,l}}{g_{ds,il}} = \frac{300}{3.14} > 95.5.$$




gm / gds for load transistors

$$L_l = 375nm.$$

- From $CMIR_{HIGH}$ spec, applying KVL:

$$CMIR_{HIGH} = V_{DD} + V_{GS,i} - V_{DS,i} - |V_{GS,l}|.$$

 - $CMIR_{HIGH,min} = 1.5V, V_{DD} = 1.8V.$
- $V_{GS,i}$ can be obtained from VGS vs gm / ID plot.




$$V_{GS,i} = 0.82V$$

- Roughly talking, $V_{DS,i} = V_i^* = \frac{2}{g_m/I_D(i)} = 0.125V.$

$$|V_{GS,l,max}| = 0.995V.$$

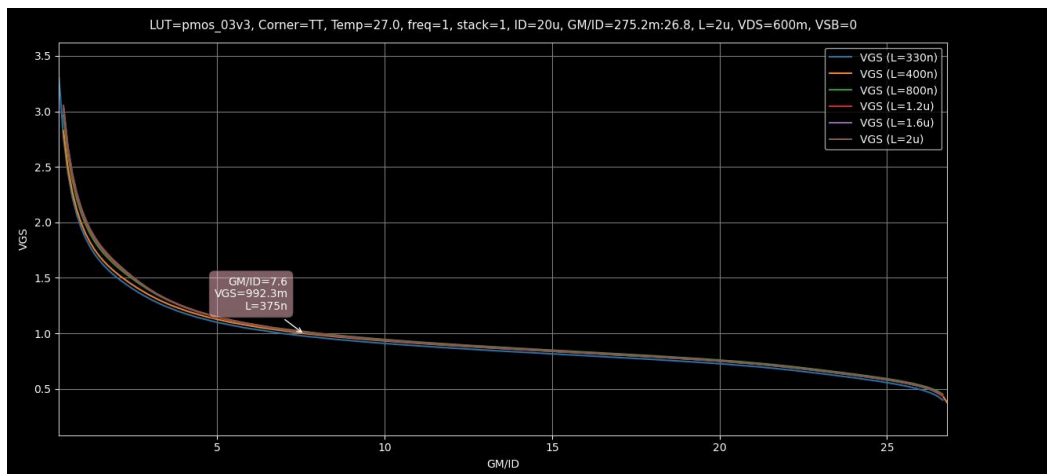
- From VGS vs gm/ID plot, a minima of $\frac{g_m}{I_D}(l)$ can be obtained.



VGS vs gm / ID for load transistors

$$\frac{g_m}{I_D}(l, \min) = 6.7S/A.$$

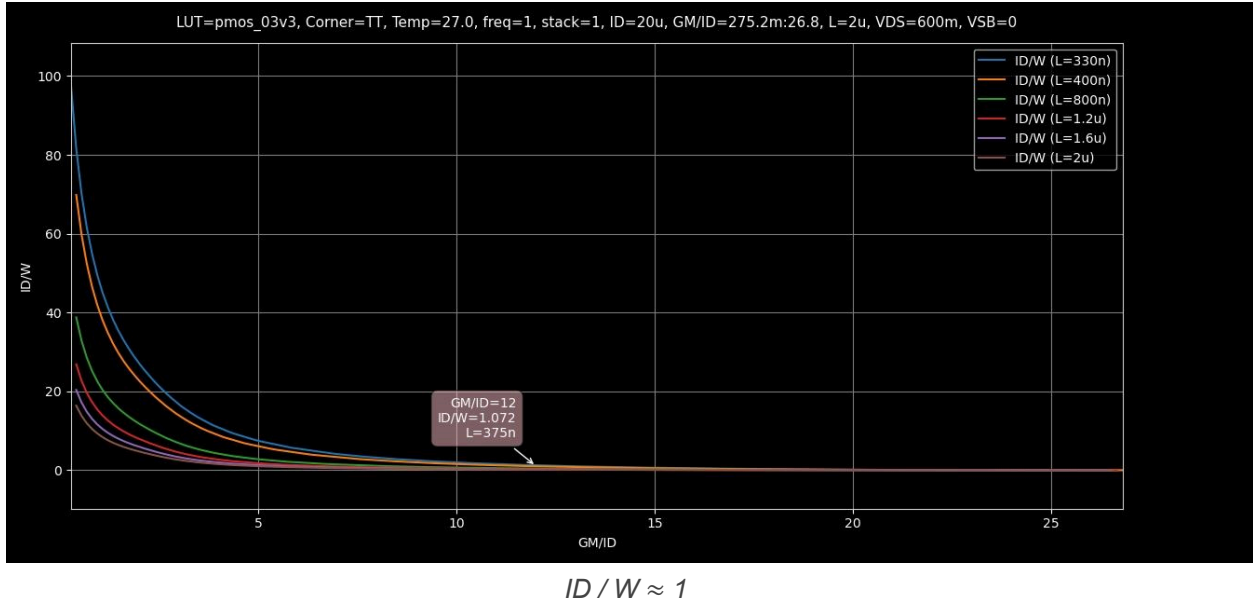- Let $\frac{g_m}{I_D}(l) = 12S/A$.
- W can be obtained from current driving capability plot.



$$W_l = 20u / 1 \approx 20um.$$


3. Design of Tail Current Source

- From $CMRR$ spec:
 $CMRR = A_{vd,dB} - A_{vCM,dB} \Leftrightarrow 34 - A_{vCM,dB} = 74 \Rightarrow A_{vCM,dB} = -40dB.$
- $A_{vCM} = \frac{1}{2g_{m,l}r_{o,tcs}} = 0.01, g_{m,l} = 300uS$, thus

$$g_{ds,tcs} < 6uS.$$

- Let $\frac{g_m}{I_D}(tcs) = 15 \Rightarrow g_{m,tcs} = 600uS$, thus

$$\frac{g_m}{g_{ds}}(tcs) > 100.$$

 


L is chosen to be 445nm

- From $CMIR_{LOW}$ spec, applying KVL: $CMIR_{LOW} = V_{GS,i} + V_{Dsat,tcs}$.
 - $CMIR_{LOW} = V$, $V_{GS,i} = 0.82V$, thus


$$V_{Dsat,tcs,max} = 0.18V.$$

- From V_{dsat} vs gm / ID plot..

 

$$gm / ID (max) = 9.3 \text{ S/A}$$

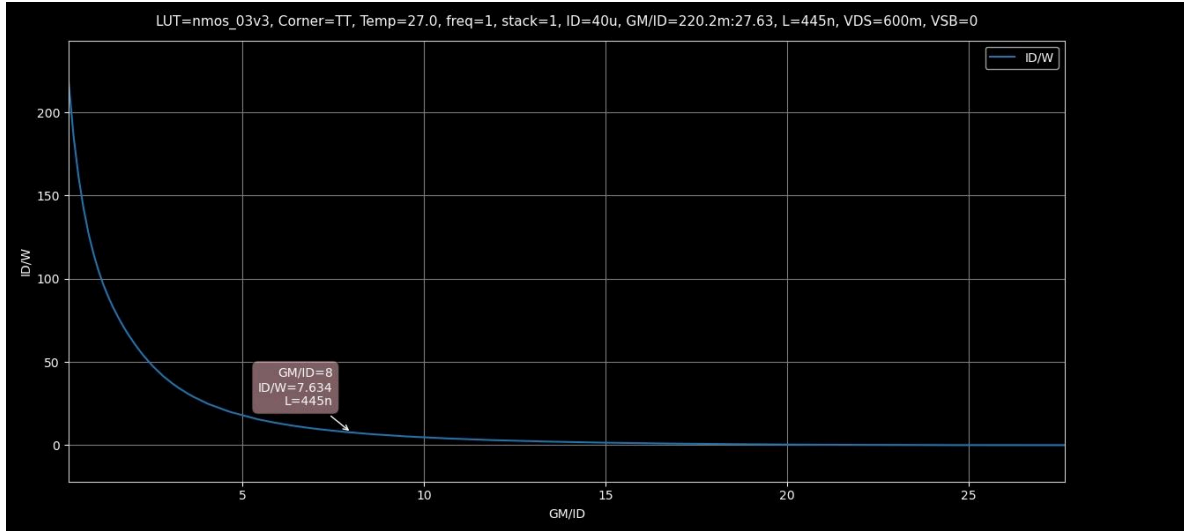- To take some margin, let $\frac{g_m}{I_D} (tcs) = 8$.
- W can be obtained from the current driving capability plot



$$ID / W = 7.6$$


$$W_{tcs} = 40u / 7.6 = 5.3um.$$

- Report a table showing W , L , g_m , I_D , g_m/I_D , V_{dsat} , $V_{ov} = V_{gs} - V_{th}$, and $V^* = 2 * g_m/I_D$ of all transistors (as calculated from g_m/I_D curves).

	W	L	g_m	I_D	g_m/I_D	$V_{dsat} \approx V^*$
i_1	17.5u	450n	314u	20u	16	0.125
i_2	17.5u	450n	314u	20u	16	0.125
l_1	20u	375n	300u	20u	12	0.167
l_2	20u	375n	300u	20u	12	0.167
tcs	5.3u	445n	600u	40u	8	0.25

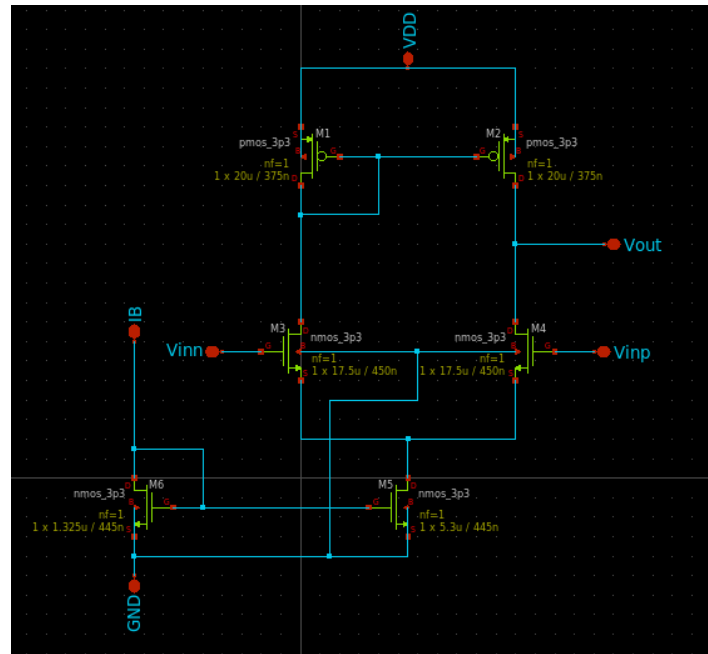Part 3: Open Loop OTA Simulation

- Create a testbench as shown above. Report the following:
 → Schematic of the OTA showing sizing of the transistors.



Required schematic


- Use VICM at the middle of the CMIR and show the operating points.

```
f2 = 1.911893e+05
peak = 5.930119e+01
f2 = 1.911893e+05
gbw = 1.133775e+07
BSIM4v5: Berkeley Short Channel IGFET Model-4
device m.x1.m.xm6.m0 m.x1.m.xm5.m0 m.x1.m.xm4.m0
model x1:nmos_3p3.8 x1:nmos_3p3.8 x1:nmos_3p3.12
gm 7.92652e-05 0.000314058 0.0003679
gmbs 2.7031e-05 0.000106251 9.77933e-05
gds 8.84883e-07 5.73422e-06 4.58001e-06
vds 0 0 0
vdsat 0.213794 0.204533 0.0789614
vgs 0 0 0
vth 0.693422 0.704402 0.834003
id 1e-05 3.8872e-05 1.9436e-05
BSIM4v5: Berkeley Short Channel IGFET Model-4
device m.x1.m.xm3.m0 m.x1.m.xm2.m0 m.x1.m.xm1.m0
model x1:nmos_3p3.12 x1:pmos_3p3.8 x1:pmos_3p3.8
gm 0.0003679 0.000121362 0.000121362
gmbs 9.77933e-05 4.90962e-05 4.90962e-05
gds 4.58001e-06 1.58333e-06 1.58333e-06
vds 0 0 0
vdsat 0.0789614 0.274487 0.274487
vgs 0 0 0
vth 0.834003 0.770999 0.770999
id 1.9436e-05 1.9436e-05 1.9436e-05
```


OP

- Note that this OP is obtained after performing fine tuning for the i/p pair, as the GBW spec was not satisfied. In order to increase GBW, G_m needs to be increased, i.e. using
 
$$\text{larger } \frac{g_m}{I_D} \cdot \frac{g_m}{I_D} = 19 \text{ is the new value used}$$




gm / gds of the i/p pair after tuning

 


ID / W of the i/p pair after tuning, $W \approx 39\mu\text{m}$.

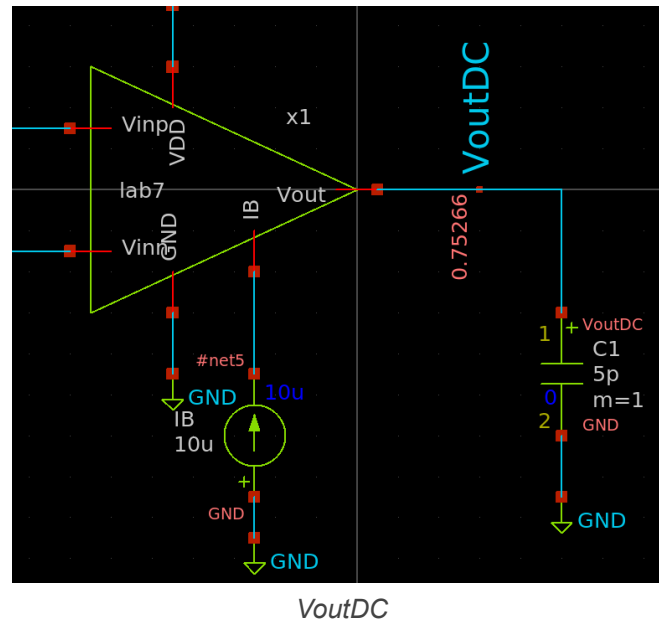- ☐ Is the current (and gm) in the input pair exactly equal?
- Yes.
- ☐ What is DC voltage at VOUT? Why?



 - It's less than the CM i/p due to CM rejection.
- Diff small signal ccs:
- ☐ Set VIDAC = 1 and VICMAC = 0. Use VICM at the middle of the CMIR. Plot diff gain (in dB) vs frequency.




Differential gain vs frequency in dB

- Compare simulation results with hand calculations in a table.

Quantity	Calculated	Simulated
A_{vd}	$A_{vd} = g_{m,i}(r_{o,i} r_{o,l})$ $= 59.72 = 35.52dB$	35.46dB

→ CM small signal ccs:

 - Use AC analysis (1Hz:10GHz, logarithmic, 10 points/decade). Set VICMAC = 1 and VIDAC = 0. Use VICM at the middle of the CMIR. Plot CM gain in dB vs frequency.



CM gain vs frequency

- Compare simulation results with hand calculations in a table.

Quantity	Calculated	Simulated
A_{vCM}	$A_{vCM} = \frac{1}{2g_{m,l}r_{o,tcs}}$ $= 0.01 = -39.2dB$	$-41.5dB$

- Note that this value was obtained after using $W_{tcs} = 470nm$ rather than the calculated one, that is, $W_{tcs,old} = 445nm$, as A_{vCM} that is needed to achieve $CMRR$ spec was not met, which indicated that longer channel is essential to rise $r_{o,tcs}$.

→ CMRR:

- ☐ Use VICM at the middle of the CMIR. Plot CMRR in dB vs frequency at VICM at the middle of the CMIR.



CMRR in dB vs frequency


- ☐ Compare simulation results with hand calculations in a table.

Quantity	Calculated	Simulated
CMRR	$g_{m,i}(r_{o,i} r_{o,l}) \times 2g_{m,l}r_{o,tc}$ $= 2516 = 68dB$	77dB

- This large deviation is due to the fact that the parameter values used in hand calculations is before tuning.

→ Diff large signal ccs:

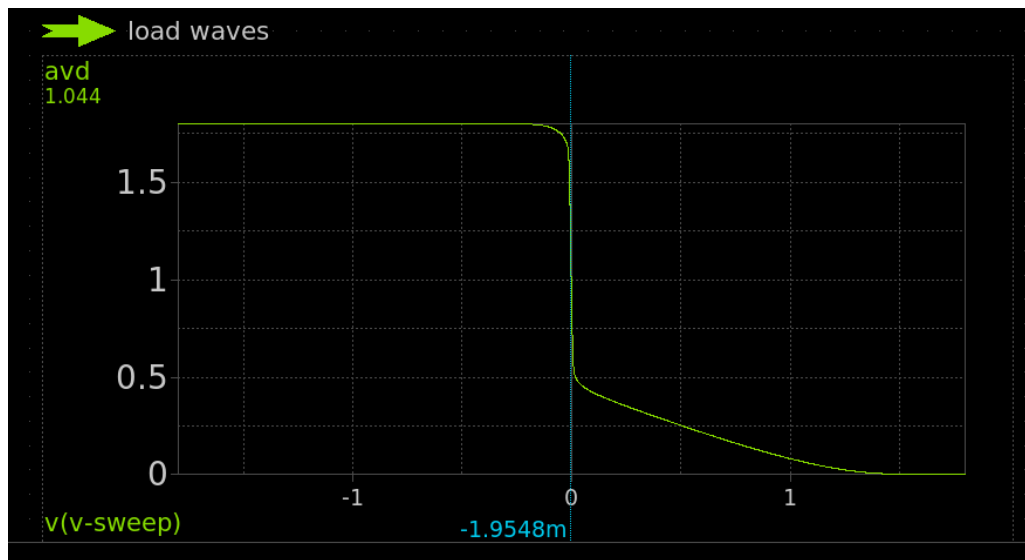
- ☐ Use VICM at the middle of the CMIR. Use DC sweep (not parametric sweep) VID = -VDD:1m: VDD. You must use a small step (1mV) because the gain region is very small (steep slope). Plot VOUT vs VID.



Vout vs VID

- ☐ From the plot, what is the value of Vout at VID = 0? Why?
 - $V_{out}(0) = 1V$.
 - To know why, values of V_{GS} and V_{DS} are required, which are not available due to SPICE code imperfections (they are shown as zeros after performing the simulation).

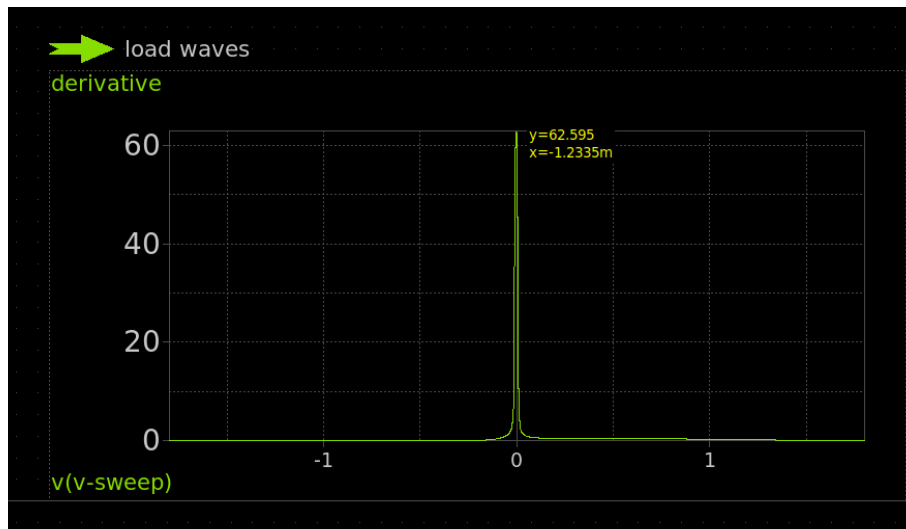- ☐ Plot the derivative of VOUT vs VID. Compare the peak with A_{vd} .




Deriv (Vout) vs VID

<i>Quantity</i>	<i>obtained from AC analysis</i>	<i>obtained from deriv plot</i>
A_{vd}	35.46dB	62.6 = 35.93dB

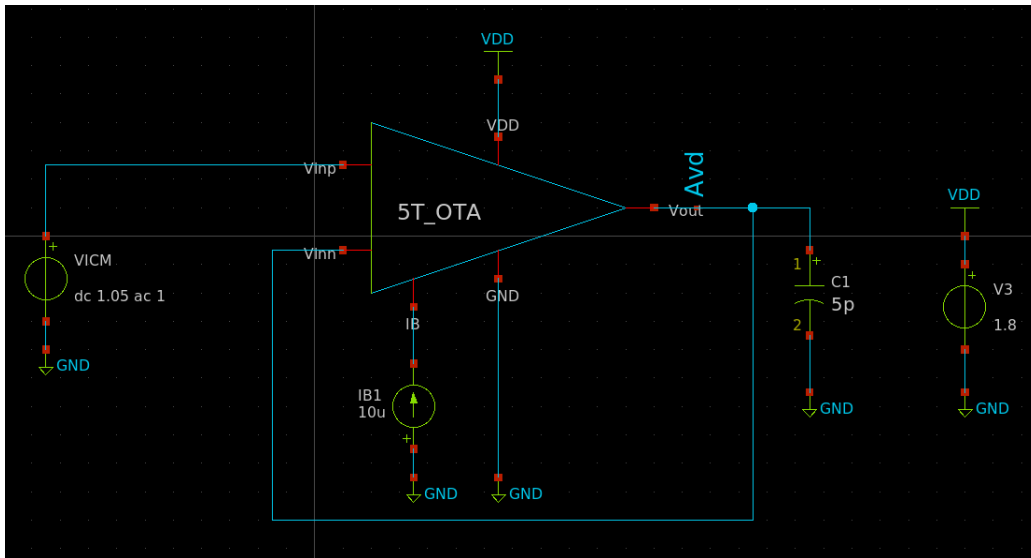Part 4: Closed Loop OTA Simulation

- Create schematic of the OTA showing current and g_m operating point. Use $V_{INCM} = CMIR_{LOW} + 50mV$.



Required schematic

```
No. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm12.m0      m.x1.xm11.m0      m.x1.xm10.m0
model       nmos_3p3.8          nmos_3p3.8          pmos_3p3.12
gm          7.74558e-05  0.000292939       0.000236479
gmbs       2.72109e-05   0.000102059       9.49974e-05
gds        7.91073e-07   1.38766e-05       2.2824e-06
vds        0.898746     0.286374          0.751887
vdsat      0.219915     0.209643          0.136693
vgs        0.898756     0.898756          0.875788
vth        0.696105     0.708302          0.775353
id         1e-05        3.76205e-05       1.86726e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm9.m0        m.x1.xm8.m0        m.x1.xm7.m0
model       pmos_3p3.12        nmos_3p3.12        nmos_3p3.12
gm          0.000239408  0.000356321       0.000360737
gmbs       9.61091e-05   0.000101684       0.000102955
gds        2.16744e-06  3.16264e-06       3.33855e-06
vds        0.875787     0.761718          0.637818
vdsat      0.137027     0.0762069         0.0767849
vgs        0.875788     0.761718          0.763608
vth        0.774881     0.791193          0.791552
id         1.89479e-05   1.86726e-05       1.89479e-05

gm_mismatch = 4.415720e-06
id_mismatch = 2.753356e-07
```

Required calculations

→ Is the current (and g_m) in the input pair exactly equal?
Why?


- There is no exact equality in I_D and g_m due to the fact that the load of one i/p transistor is a diode-connected device, which probably leads to gate current leakage that creates a non-exact equality between currents and, therefore, the transconductances.

→ Calculate the mismatch in I_D and g_m .

$$\sigma I_{out}/I_{out} = 2.75e - 7/20u = 1.375\%$$
$$\sigma g_m/g_m = 4.42e - 6/0.0003067 = 1.44\%$$


- Loop Gain:

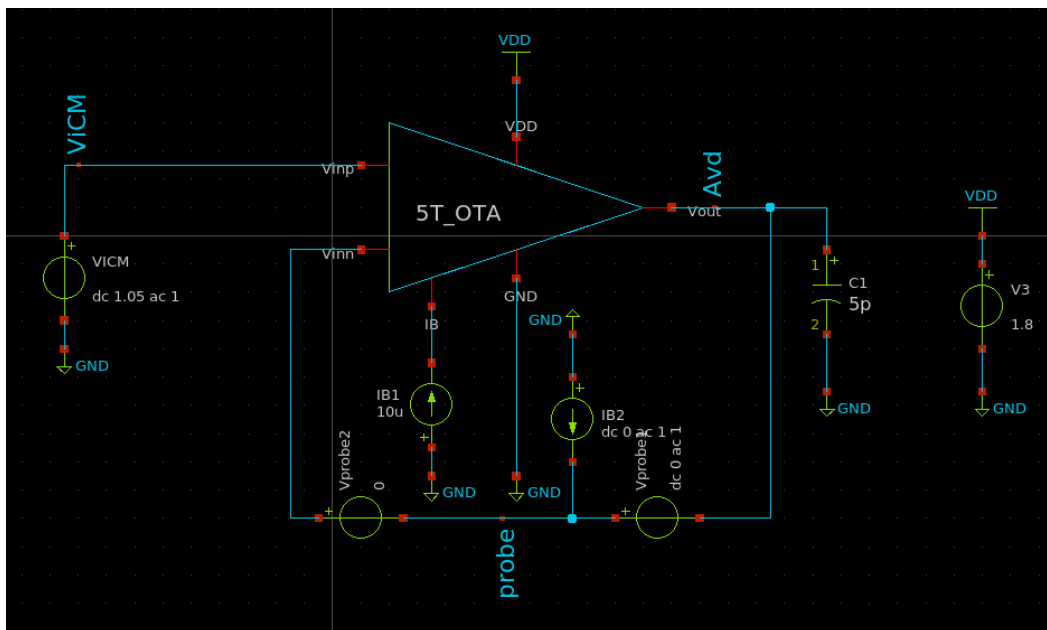→ Put the OTA in a unity gain buffer configuration as shown in the schematic below.



Required configuration

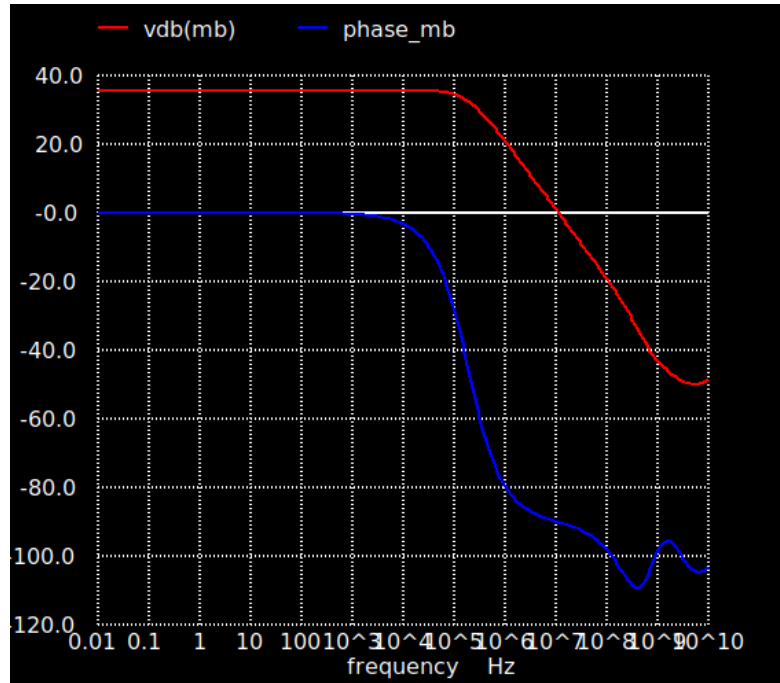→ Use VICM at the middle of the CMIR. Plot loop gain in dB and phase vs frequency. Show the results in the console.



Loop gain & phase vs frequency

```

bw          = 1.828081e+05
pm_deg      = -9.004003e+01
dominant_pole_f = 1.122027e+07
loop_gain   = 3.577049e+01
gbw = 1.123362e+07
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.m.xm6.m0      m.x1.m.xm5.m0      m.x1.m.xm4.m0
model       x1:nmos_3p3.8      x1:nmos_3p3.8      x1:nmos_3p3.12
gm          7.74558e-05        0.000307758        0.00036236
gmbs       2.72109e-05        0.000107105        9.62457e-05
gds        7.91073e-07        5.34252e-06        3.19357e-06
vds        0.898746          0.44013            0.804686
vdsat      0.219815          0.209838           0.0772391
vgs        0.898756          0.898756           0.804687
vth        0.696105          0.708033           0.83266
id         1e-05             3.88705e-05        1.90418e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.m.xm3.m0      m.x1.m.xm2.m0      m.x1.m.xm1.m0
model       x1:nmos_3p3.12      x1:pmos_3p3.12      x1:pmos_3p3.12
gm          0.00037462         0.000238164        0.000246589
gmbs       9.95332e-05        9.5786e-05         9.9002e-05
gds        3.79541e-06        2.67089e-06        2.2472e-06
vds        0.480469          0.555162           0.879379
vdsat      0.0788564         0.138713           0.139592
vgs        0.809851          0.879381           0.879381
vth        0.833653          0.776101           0.774868
id         1.98288e-05        1.90417e-05        1.98288e-05

```

Results from console

→ Compare DC gain and GBW with those obtained from open-loop simulation. Comment.

Quantity	OL	LG
DC gain	~ 59	~ 35.7dB ≈ 60.9
GBW	11.3M	11.2M

- Open loop gain and loop gain are the same as $\beta = 1$.
- Show the operating point at VICM in the middle of the CMIR.

```

No. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m,x1,m,xm6,m0      m,x1,m,xm5,m0      m,x1,m,xm4,m0
model       x1:nmos_3p3.8    x1:nmos_3p3.8    x1:nmos_3p3.12
gm          7.74558e-05   0.000307758      0.00036236
gmbs        2.72109e-05   0.000107105      9.62457e-05
gds         7.91073e-07   5.34252e-06      3.19357e-06
vds         0.898746      0.44013          0.804686
vdsat       0.219915      0.209838         0.0772391
vgs         0.898756      0.898756         0.804687
vth         0.696105      0.708033         0.83266
id          1e-05         3.88705e-05      1.90418e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m,x1,m,xm3,m0      m,x1,m,xm2,m0      m,x1,m,xm1,m0
model       x1:nmos_3p3.12    x1:pmos_3p3.12    x1:pmos_3p3.12
gm          0.00037462     0.000238164       0.000246589
gmbs        9.95332e-05   9.5786e-05        9.9002e-05
gds         3.79541e-06        2.67089e-06       2.2472e-06
vds         0.480469          0.555162          0.879379
vdsat       0.0788564       0.138713          0.139592
vgs         0.809851          0.879381          0.879381
vth         0.833653          0.776101          0.774868
id          1.98288e-05       1.90417e-05       1.98288e-05

```

OP @ middle of CMIR

→ Compare simulation results (DC gain and GBW) with hand calculations in a table.

Quantity	Calculated	Simulated
DC gain	$LG = \beta A_{OL} = A_{OL} \approx 60$	35.8dB = 60.9
GBW	$GBW(LG) = GBW(A_{OL}) = 11.3M$	11.2M