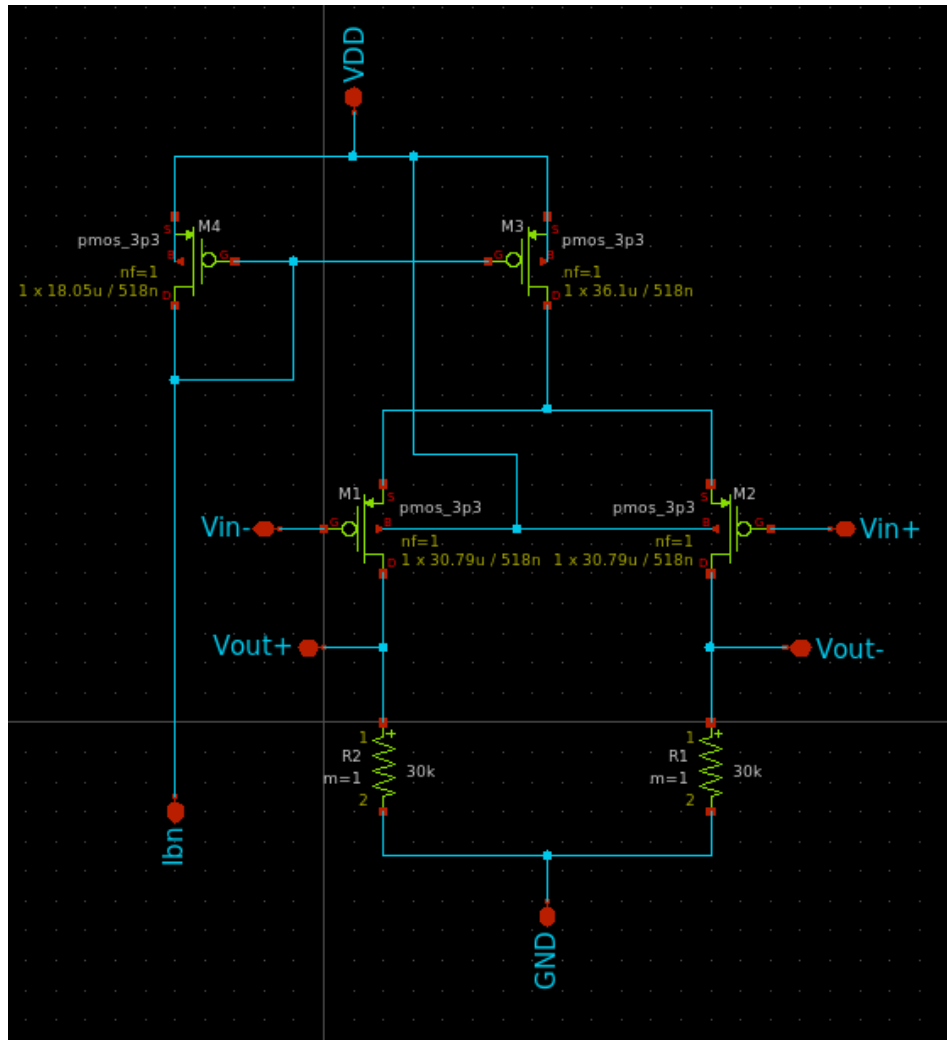


CMOS AIC design - ITI - Lab 6

Part 1: Differential Amplifier Design



Required schematic

- Choose R_D to meet the CM output level spec.

$$R_D = \frac{V_{DD}/3}{I_{SS}/2} = 30k\Omega.$$

- Choose V^* to meet the differential gain spec.

$$V^* = \frac{1.82V_{RD}}{|A_v|} \approx 135mV.$$

- Assume we will set V_{DS} of the tail current source to $300mV$ to allow more output swing. Report the input pair sizing using SA.

L	350n
W	30.79u


i/p pair sizing

- Given the above assumption for V_{DS} of the tail current source, calculate the required CM input level.


$$V_{i,CM} = V_{DD} - V_{GS,i} - V_{DS,tcs} = 0.56V$$

*Data from ADT **

 
- Use SA to plot the sizing at a constant $\sigma I_{out}/I_{out}$.



*L vs V**

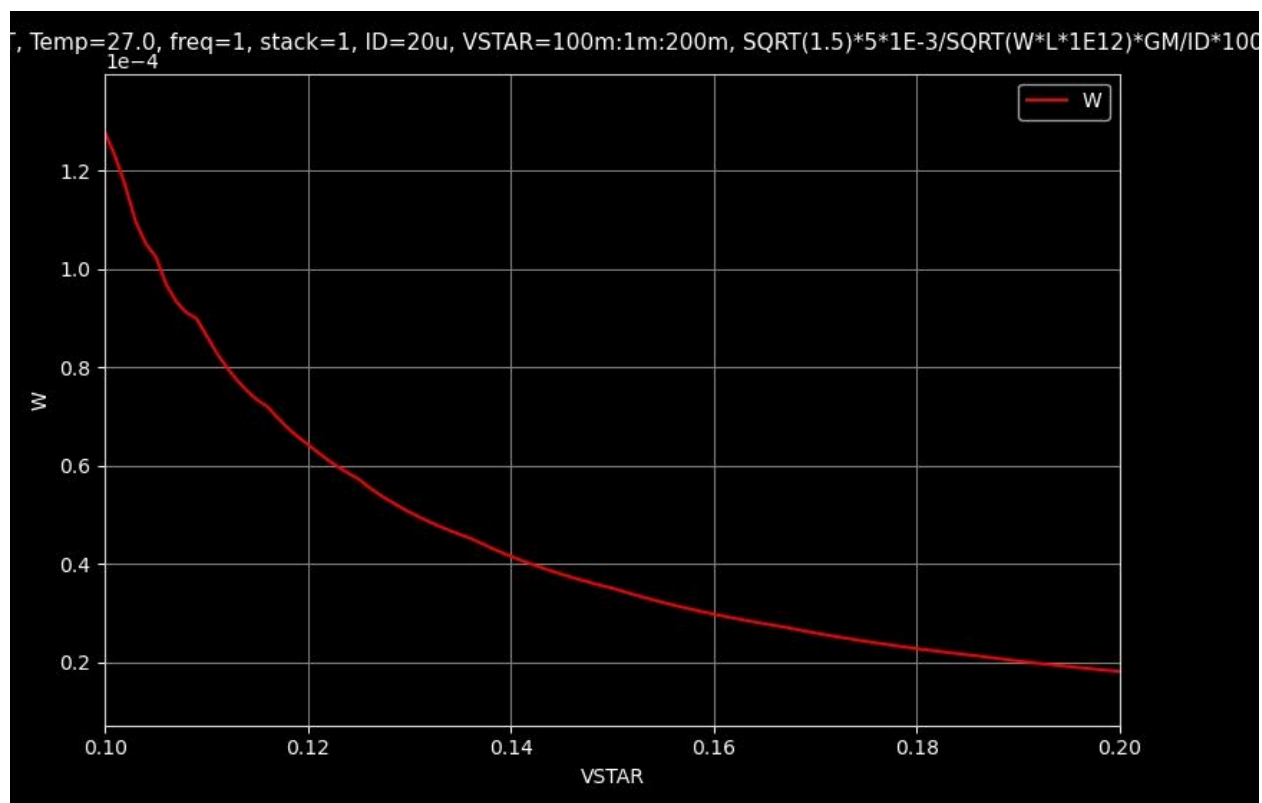


W vs V^*

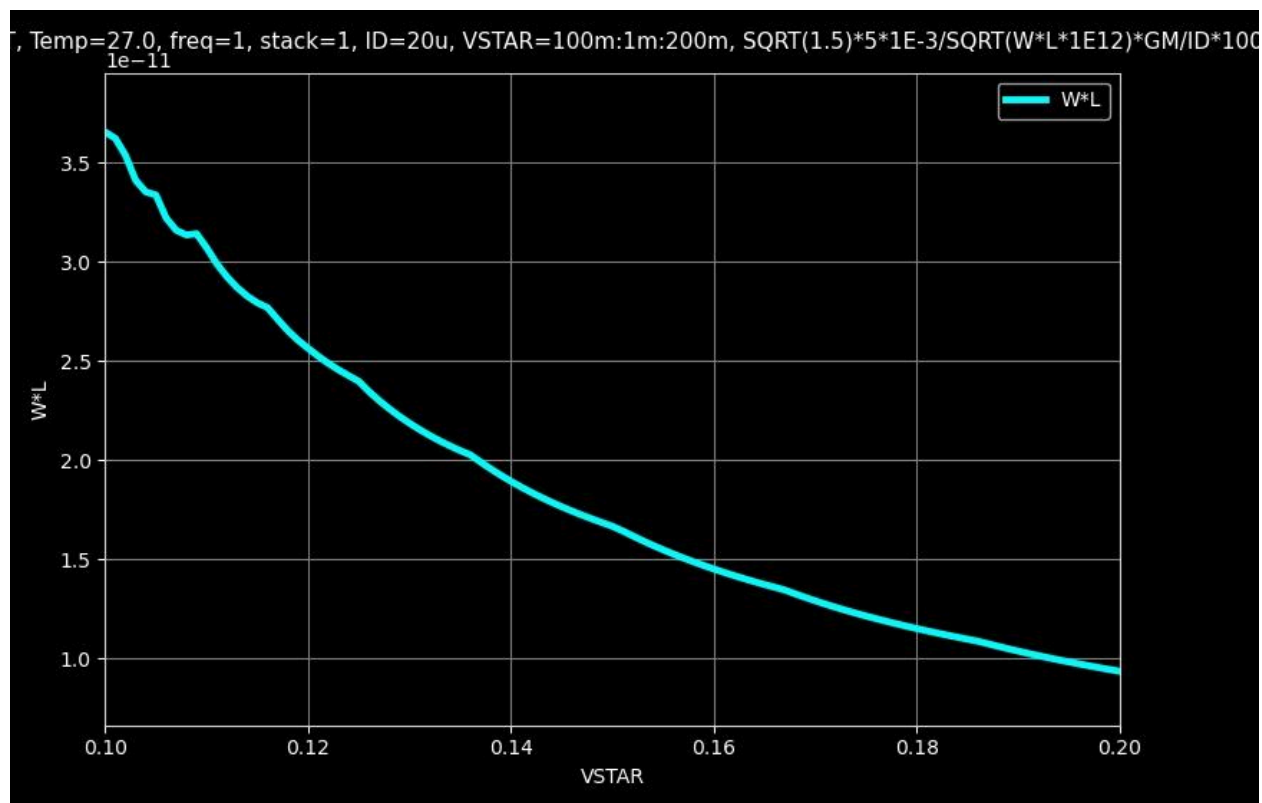


Area vs V^*

 
- Given the compliance voltage spec, report the above figure with a cursor added to the selected design point.



L @ selected design point

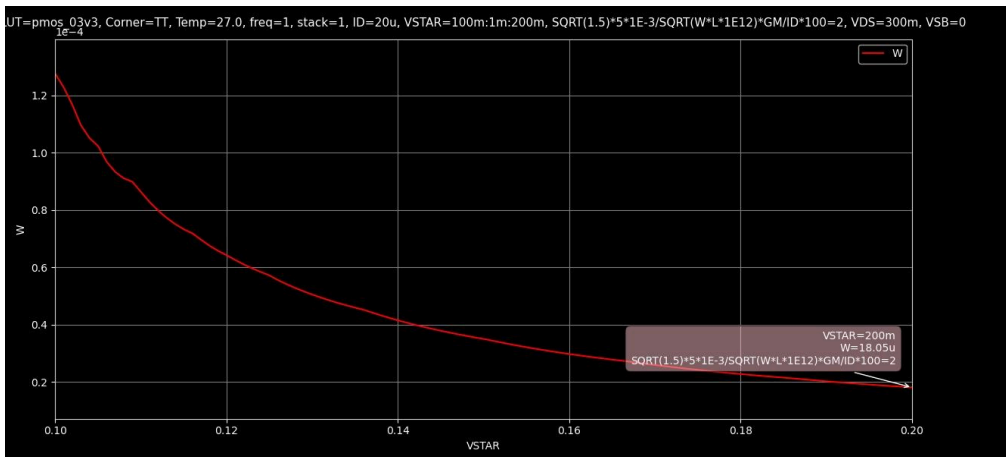

W @ selected design point

 

Area @ selected design point

- Calculate the min and max CM input levels. Is the previously selected CM input level in the valid range?


$$V_{i,CM,min} = V_{th,i} + V_O = -270mV.$$

$$V_{i,CM,max} = -V_{GS,i} - V^* + V_{DD} = 0.66V.$$

- The selected CM i/p **is** in the valid range.

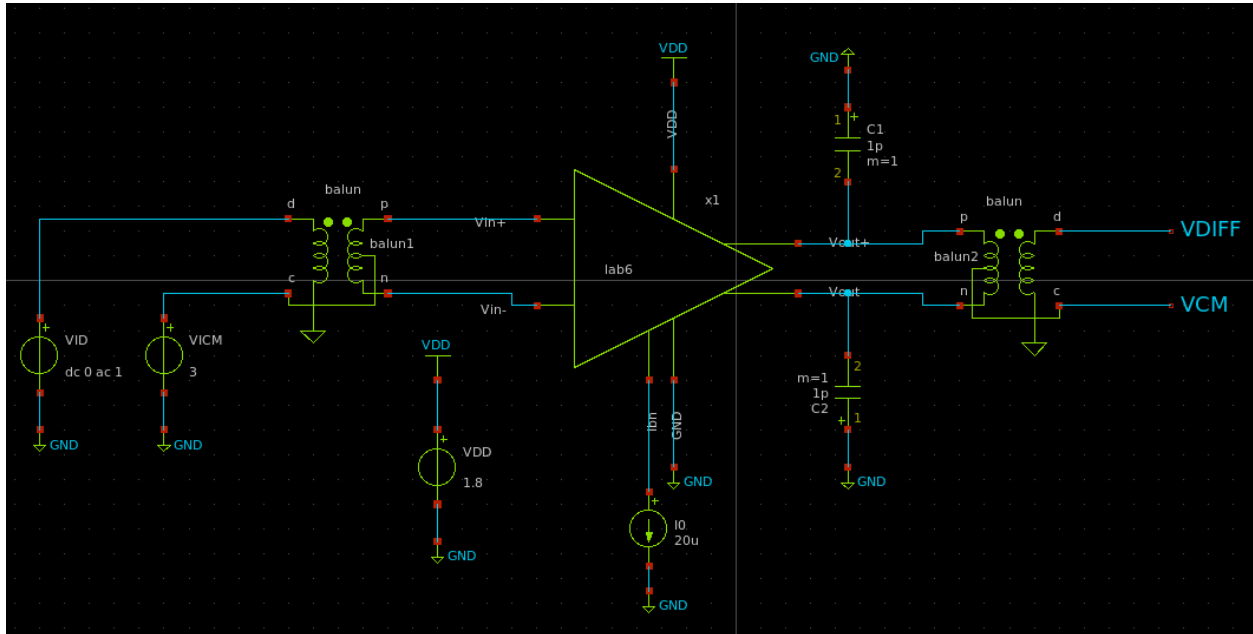Part 2: Differential Amplifier Simulation

- Create the schematic of a differential amplifier “lab_06_diff_amp”. Create a symbol for the diff pair. Edit the symbol to look as shown below in the testbench schematic. Create a new cell for the testbench “lab_06_diff_amp_tb”. Create the testbench schematic as shown below.



Required schematic

- Report OP simulation

→ Report a snapshot clearly showing the following parameters.

```
No. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m,x1,m,xm4,m0      m,x1,m,xm3,m0      m,x1,m,xm2,m0
  model      x1:pmos_3p3.13      x1:pmos_3p3.13      x1:pmos_3p3.13
  id          2e-05              3.77022e-05          1.85842e-05
  gm          0.000205329         0.000394098          0.000238335
  gds         1.01639e-06         2.45003e-06          1.39868e-06
  gmbs        9.19315e-05         0.000176478          7.83489e-05
  vgs         0.9381             0.9381               1.14067
  vth         0.787552           0.79174              1.04167
  vds         0.938098           0.659327             0.583145
  vdsat       0.16612            0.163028             0.140964


BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m,x1,m,xm1,m0
  model      x1:pmos_3p3.13
  id          1.9118e-05
  gm          0.000242765
  gds         1.46266e-06
  gmbs        7.98073e-05
  vgs         1.14067
  vth         1.03944
  vds         0.567129
  vdsat       0.142613
```

OP simulation results

→ Check that all transistors operate in saturation.

#	V_{DS}	V_{Dsat}	<i>Sat?</i>
1	0.6	0.14	<i>Yes</i>
2	0.6	0.14	<i>Yes</i>
3	0.66	0.16	<i>Yes</i>
4	0.94	0.17	<i>Yes</i>

 - Diff small signal ccs:
 - Report the Bode plot of small signal diff gain.



Bode mag plot of diff gain

No. of Data Rows : 101

gain = 7.087708e+00 at= 1.000000e+00

bw = 5.351974e+06


Required calculations

→ Compare the DC diff gain and BW with hand analysis in a table.

Quantity	Calculated	Simulated
Gain	$A_v = g_{m,i}(R_D r_o)$ ≈ 7	$A_v = 7.09$
BW	$BW = \frac{1}{R_o C_o}$ $\approx 5.46 \text{ MHz}$	$BW = 5.35 \text{ MHz}$

- CM small signal ccs:

 → Report the Bode plot of small signal CM gain.



Bode mag plot of small signal CM gain

```
No. of Data Rows : 101
cmgain          = 2.887720e-02 at= 1.000000e+00
CM gain
```

→ Compare the DC CM gain with hand analysis in a table. Is it smaller than “1”? Why?


Quantity	Calculated	Simulated
Gain	$A_v = \frac{g_{m,i}}{1+2g_{m,i}r_{o,tcs}} (R_D r_o)$ $\approx 26.4m$	$A_v = 28.8m$

- It's smaller than 1, as the value of the degeneration resistance " $2R_{ss} = 2r_{o,tcs} \approx 400k\Omega$ " is very large.

→ Justify the variation of A_{vcm} vs frequency.

- A_{vCM} varies with frequency due to the fact that the capacitances of the tail current source shunt R_{ss} at high frequencies.

 → Plot A_{vd}/A_{vcm} in dB. Compare A_{vd}/A_{vcm} @ DC with hand analysis in a table.



CMRR in dB vs frequency

```
No. of Data Rows : 91
cmgain          = 2.973648e-02 at= 1.995262e+00
diffgain        = 7.228935e+00 at= 1.000000e+00
cmrr val = 2.430999e+02
```


CMRR

Quantity	Calculated	Simulated
CMRR	$CMRR = 2(g_{m,i} + g_{mb,i})R_{ss}$ ≈ 227	$CMRR = 243$

- Justify the variation of A_{vd}/A_{vcm} with frequency.
- CMRR is proportional to R_{ss} and R_{ss} decreases with frequency due to C_p .

- Diff large signal ccs:

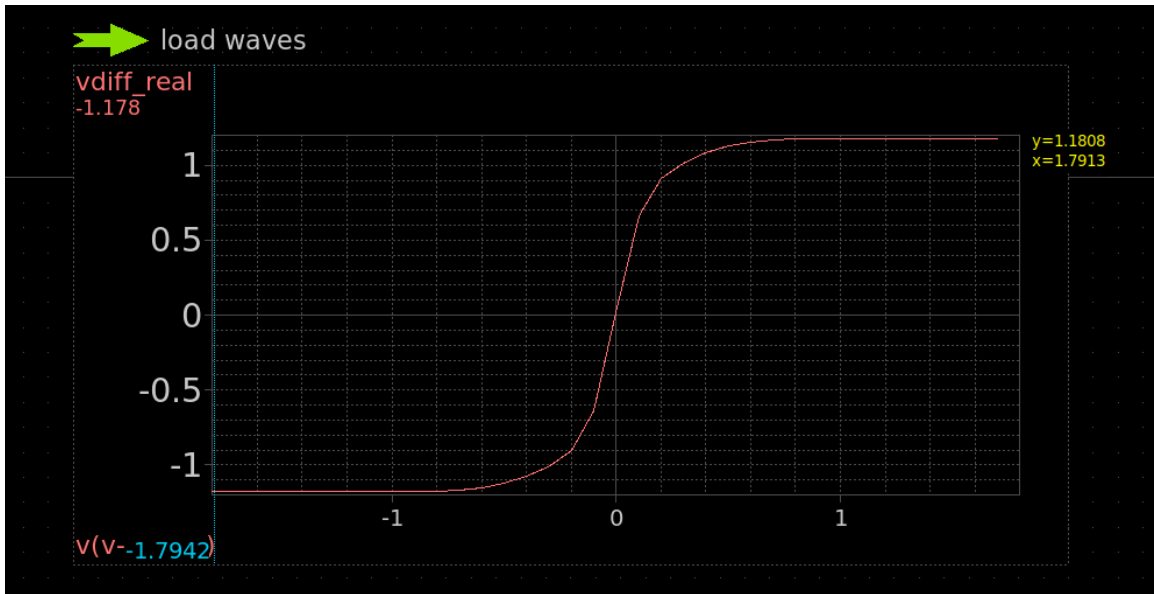- Report diff large signal ccs (VODIFF vs VIDIFF). Compare the extreme values with hand analysis in a table.




Vod vs Vid

Quantity	Calculated	Simulated
$ I_{ss}R_D $	1.131	1.18

- CM large signal ccs (GBW vs Vicm):

 - Report CM large signal ccs (GBW vs VICM). Assume the valid range for Vicm (CMIR) is defined by the condition that A_{vd} is within 90% of the max gain, i.e., 10% drop in gain.



GBW vs V_{iCM}

→ Find the CM input range (CMIR). Compare with hand analysis in a table.

```
vicmmax = 6.600000e-01
vicmmin = -4.600000e-01
```

CMIR

Quantity	Calculated	Simulated
CMIR	$-270m < V_{iCM} < 0.66$	$-460m < V_{iCM} < 660m$