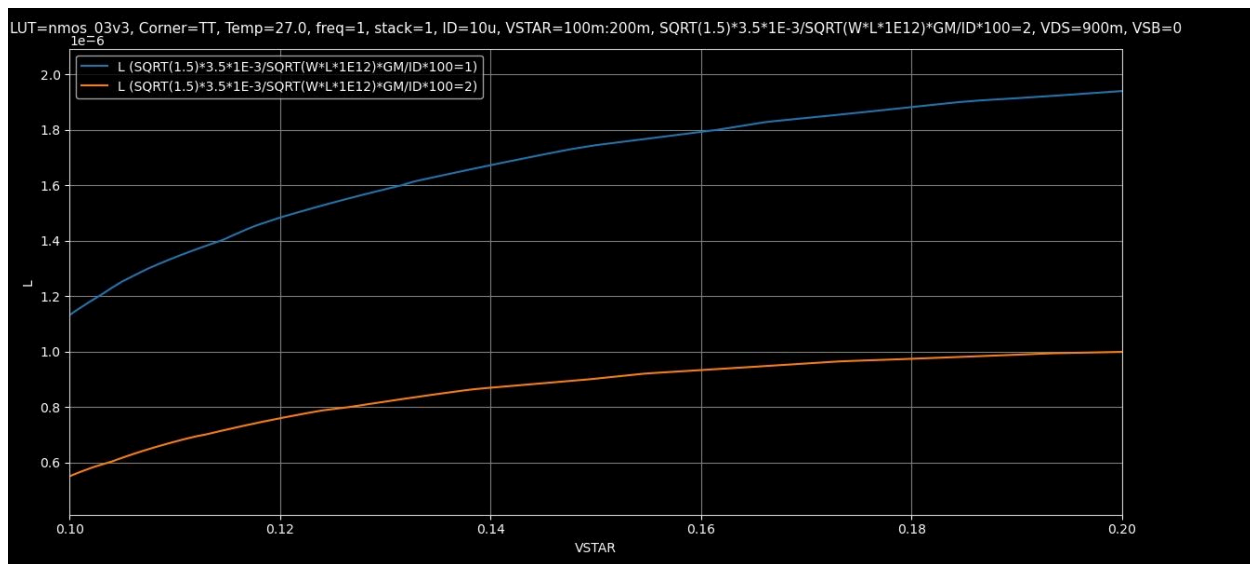


CMOS AIC design - ITI - Lab 5


Part 1: Exploring Sizing Tradeoffs Using SA

- Sinking current means which device type? NMOS or PMOS?
 - Sinking current is performed using NMOS.
- The % Change in current translates to a spec on the $\lambda = 1/V_A$ of the device. How much is the required λ ?


$$I_D = I_{DS}(1 + \lambda V_{DS}), \quad \left. \frac{\Delta I_D}{\Delta V_{DS}} \right|_{V_{DS}=1} = \lambda \frac{I_D}{1+\lambda} \Rightarrow \lambda = 0.1$$




L vs V*

 

W vs V^*

 


Area vs V^*

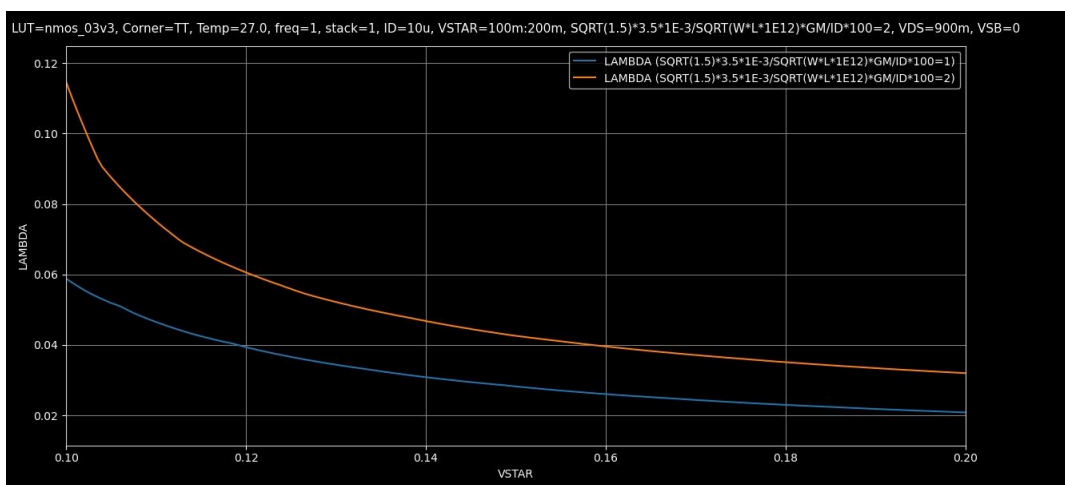


Lambda vs V^*

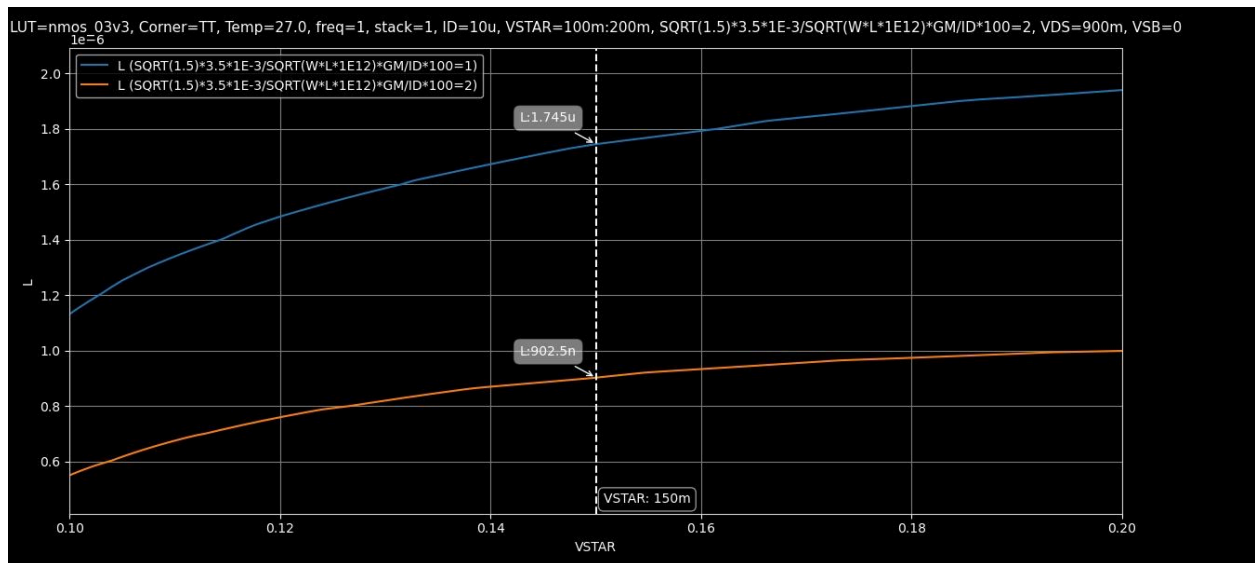
- Can we do the previous design trade-offs exploration sweeps using a standard SPICE simulator, i.e., sweep V_{star} at a constant $\sigma(I_{out})/I_{out}$? Why?
 - The mismatch is a statistical measure which the standard SPICE simulator has no control over.
- Report the above plot with a cursor added at the required V^* . Does this point satisfy the mismatch and λ constraints?




$L @ \text{required } V^*$

 

$W @ \text{required } V^*$

 

Area @ required V^*

 

Lambda @ required V^*

- The constraints are satisfied.
- If the λ constraint is not satisfied at $\sigma(I_{out})/I_{out}=2\%$, i.e., it needs a longer L , we can use SA to find the required design point as shown below. Report the device sizing and $\sigma(I_{out})/I_{out}$ at the selected design point.

L

470n


W

4.79u

Device sizing after redesign

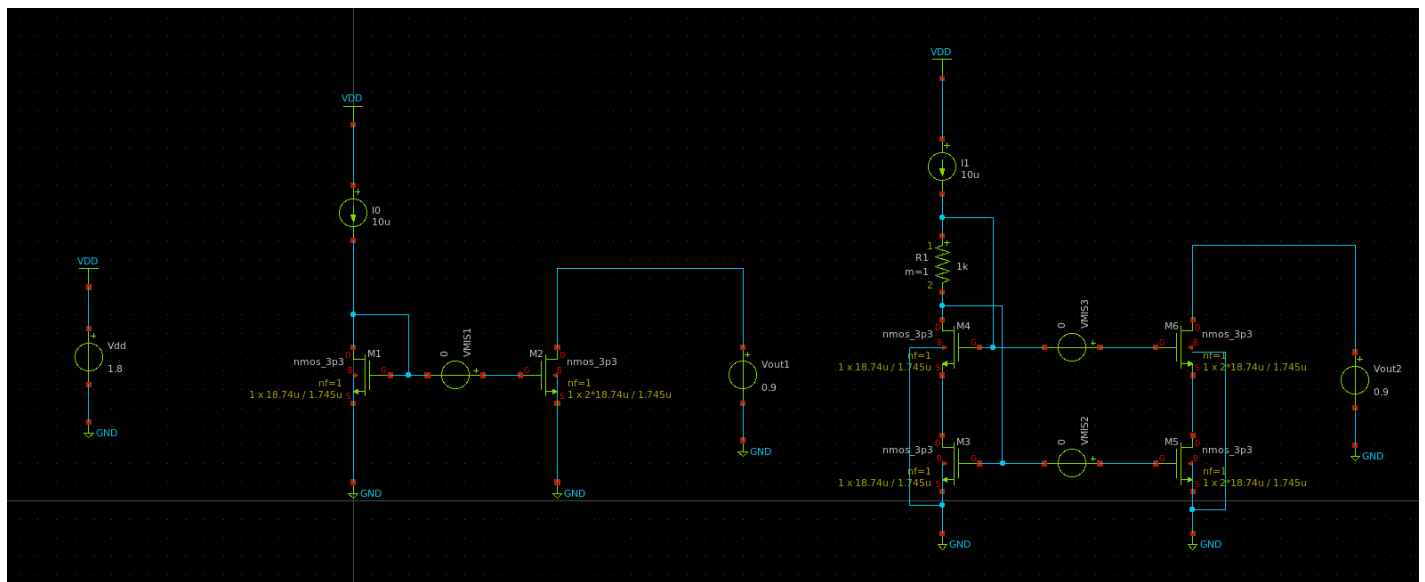Part 2: Current Mirror Simulation

- Create a new schematic. Construct the circuit shown below.



Required schematic

1. Design and OP (Operating Point) Analysis

- Assume we want to set a 50mV saturation margin for M6 and M3, i.e., $V_{DS6} \approx V_{DS3} \approx V^* + 50mV$. Ignore the body effect and calculate a rough value for RB.

$$R_B = \frac{200m}{10u} = 20k\Omega.$$

- Perform DC sweep (not parametric sweep) for R_B . Choose a reasonable sweep range given the rough value computed in the previous step. Report V_{DS6} vs R_B . Choose R_B to satisfy the 50mV saturation margin requirement. Is the selected R_B value larger or smaller than the rough analytical value? Why?


```
No. of Data Rows : 31
binary raw file "CM_TB_final.raw"
BSIM4v5: Berkeley Short Channel IGFET Model-4
```

| device | m.xm5.m0 | m.xm6.m0 | m.xm2.m0 |
|--------|-------------|-------------|-------------|
| model | nmos_3p3.14 | nmos_3p3.14 | nmos_3p3.14 |
| id | 1.99541e-05 | 1.99541e-05 | 1e-05 |
| gm | 0.000269502 | 0.000267681 | 0.0001349 |
| gds | 5.86337e-07 | 1.63754e-06 | 3.22657e-07 |
| vgs | 0.831469 | 0.751969 | 0.831955 |
| vth | 0.754193 | 0.672884 | 0.754132 |
| vds | 0.679499 | 0.220499 | 0.531954 |


```
BSIM4v5: Berkeley Short Channel IGFET Model-4
```

| device | m.xm3.m0 | m.xm4.m0 | m.xm1.m0 |
|--------|-------------|-------------|-------------|
| model | nmos_3p3.14 | nmos_3p3.14 | nmos_3p3.14 |
| id | 1e-05 | 2.05127e-05 | 1e-05 |
| gm | 0.000134025 | 0.000273983 | 0.000134595 |
| gds | 8.2581e-07 | 5.67682e-07 | 2.92144e-07 |
| vgs | 0.751969 | 0.751426 | 0.751426 |
| vth | 0.672671 | 0.672136 | 0.673656 |
| vds | 0.220013 | 0.899999 | 0.751425 |

Required calculations

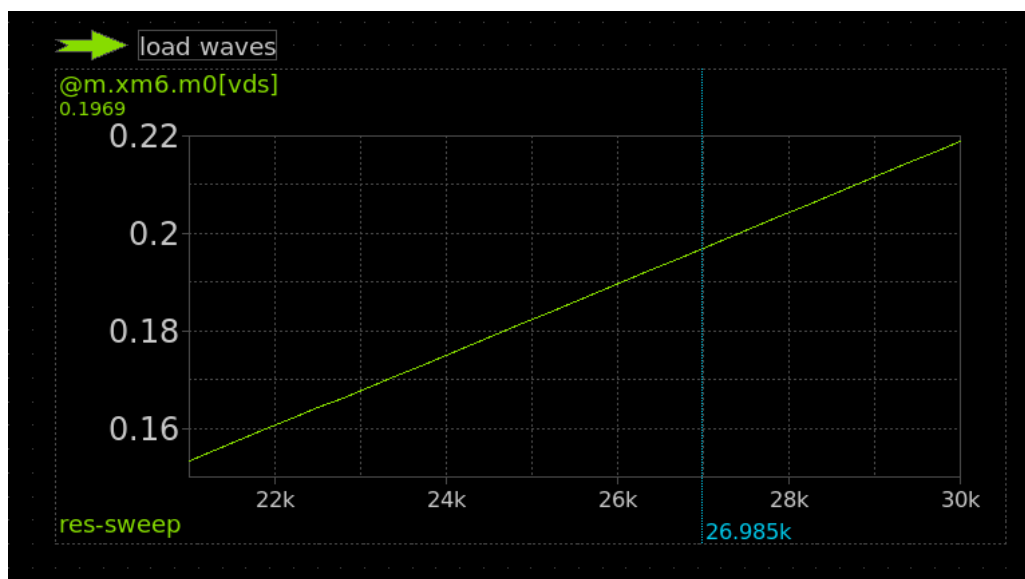

Required $R_B \approx 27k\Omega$

- The selected R_B has a larger value than the roughly-estimated one due to approximations implied in hand analysis.
- Simulate the OP point. Report a snapshot clearly showing the following parameters.

No. of Data Rows : 1

BSIM4v5: Berkeley Short Channel IGFET Model-4

| | | | |
|--------|-------------|-------------|-------------|
| device | m.xm5.m0 | m.xm6.m0 | m.xm2.m0 |
| model | nmos_3p3.14 | nmos_3p3.14 | nmos_3p3.14 |
| id | 1.99268e-05 | 1.99268e-05 | 1e-05 |
| gm | 0.000269042 | 0.000262934 | 0.000134798 |
| gds | 5.72584e-07 | 8.03127e-06 | 3.0815e-07 |
| vgs | 0.805508 | 0.752625 | 0.807068 |
| vth | 0.72841 | 0.6727 | 0.72932 |
| vds | 0.752881 | 0.147116 | 0.607067 |
| vdsat | 0.116533 | 0.116431 | 0.116917 |
| gmbs | 9.82432e-05 | 0.000103149 | 4.92533e-05 |

BSIM4v5: Berkeley Short Channel IGFET Model-4

| | | | |
|--------|-------------|-------------|-------------|
| device | m.xm3.m0 | m.xm4.m0 | m.xm1.m0 |
| model | nmos_3p3.14 | nmos_3p3.14 | nmos_3p3.14 |
| id | 1e-05 | 1.97421e-05 | 1e-05 |
| gm | 0.000131593 | 0.000266887 | 0.000134613 |
| gds | 4.30677e-06 | 5.52745e-07 | 2.92492e-07 |
| vgs | 0.752625 | 0.748558 | 0.748558 |
| vth | 0.672335 | 0.672118 | 0.670807 |
| vds | 0.145556 | 0.899999 | 0.748557 |
| vdsat | 0.116655 | 0.114304 | 0.115101 |
| gmbs | 5.16262e-05 | 0.000104682 | 5.27906e-05 |


Required calculations

- Do all transistors operate in saturation?


| # | V_{DS} | $V_{DS,sat}$ | Sat? |
|---|----------|--------------|------|
| 1 | 0.75 | 0.11 | Yes |
| 2 | 0.6 | 0.11 | Yes |
| 3 | 0.15 | 0.11 | Yes |
| 4 | 0.9 | 0.11 | Yes |
| 5 | 0.75 | 0.11 | Yes |
| 6 | 0.15 | 0.11 | Yes |

 2. DC Sweep (I_{out} vs $VOUT$)

- Perform DC sweep (not parametric sweep) using $VOUT = 0:10m:VDD$. Report I_{out} vs $VOUT$ for the two CMs overlaid in the same plot. Comment on the difference between the two circuits.




I_{out1} vs V_{out1}

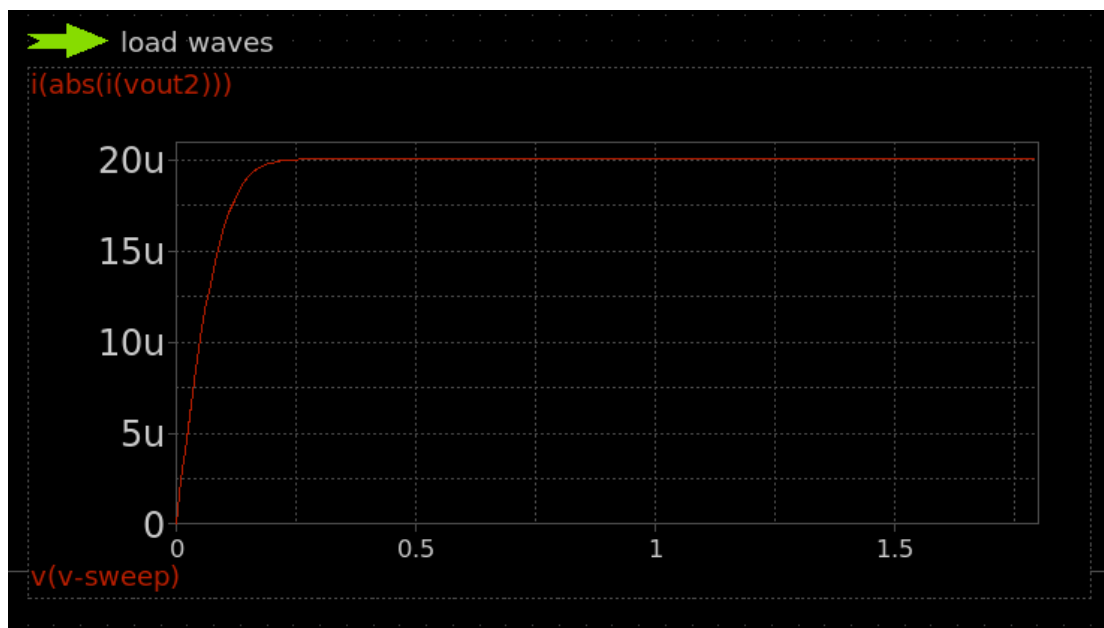


I_{out2} vs V_{out2}

 - It's clear that the wide swing CM acts as a current source more ideal than the conventional CM due to the boosted o/p impedance.
- From the plot, find an estimate for the compliance voltage of each current mirror.




 Compliance voltage of the conventional CM




Compliance voltage of the wide swing CM

 - I_{out} of the simple CM is exactly equal to $I_B \cdot 2$ at a specific value of V_{OUT} . Why?




V @ which $I_{out} \approx 2I_B$

 - I_{out} nearly equals I_{ref} @ $V_{out} \approx 1.8V = V_{DD}$ which is the maximum V_{out} obtainable that achieves the almost-ideal current mirroring.
- For the simple current mirror, calculate the percent change in I_{out} when V_{OUT} changes from 0.5V to 1.5V (i.e., 1V change). Compare the result to the value expected from Part 1.




I_{out} @ $V_{out} = 1V$

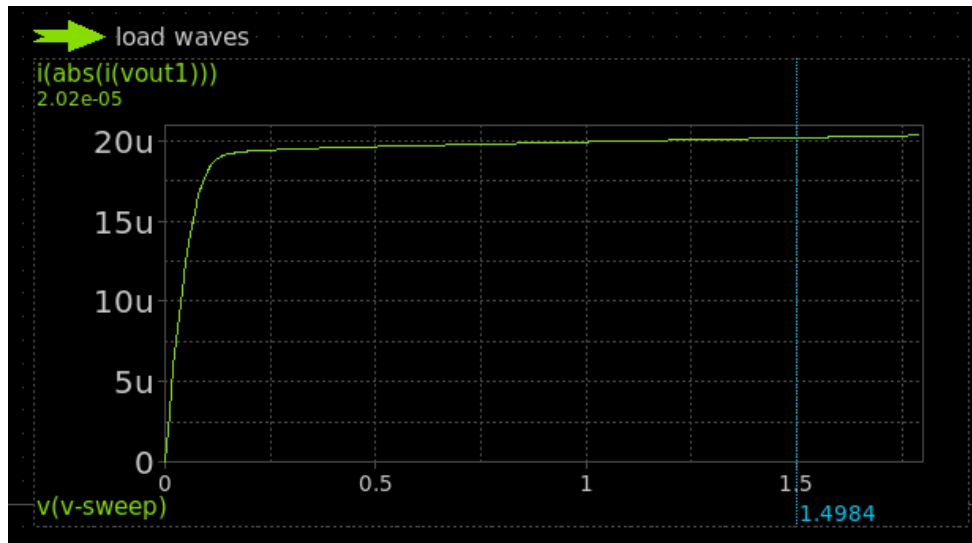

$I_{out} @ V_{out} = 1.5V$



$$\frac{\Delta I_{out}}{\Delta V_{out}} = \frac{2.02\mu - 1.99\mu}{1.5 - 1} = 60n << 0.1$$

 - Report the percent of error in I_{out} vs VOUT (ideal I_{out} should be $I_B \cdot 2$) for the two CMs in the current mirror operating region ($V_{OUT} \approx V^*$ to VDD) overlaid in the same plot. Comment on the difference between the two circuits.



Percent error in I_{out} vs V_{out}

- As V_{out} increases, the percent error in the conventional CM is getting very large compared to that of the wide swing CM.
- Report R_{out} vs V_{OUT} (take the inverse of the derivative of I_{out} plot) for the two CMs in the current mirror operating region ($V_{OUT} \approx V^*$ to V_{DD}) overlaid in the same plot. Use log scale on the y-axis. Add a cursor at $V_{OUT} = V_{DD}/2$. Comment on the difference between the two circuits. Does R_{out} change with V_{OUT} ? Why?

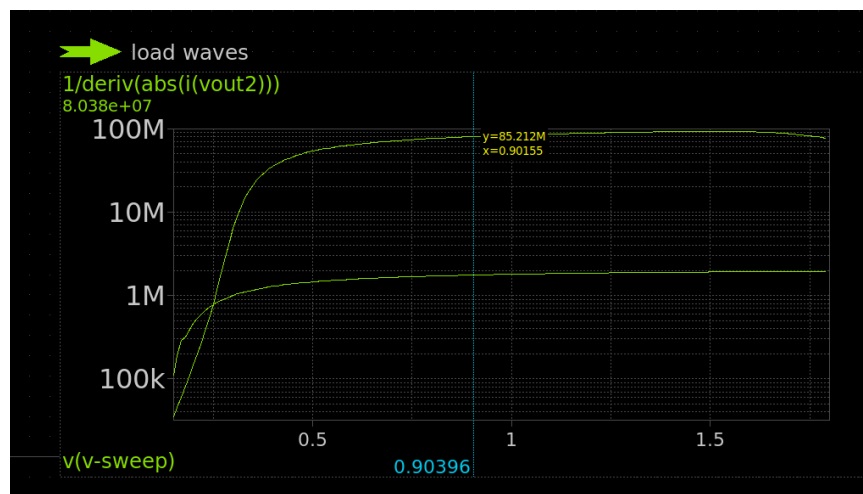 

Rout vs Vout

- The o/p impedance of the wide swing CM is much larger than that of the conventional CM.
- The variation of R_{out} with V_{out} is due to the fact that

$$R_{out} = \frac{\Delta V_{out}}{\Delta I_{out}} = f(V_{out}).$$

- Analytically calculate Rout of both circuits at VOUT = VDD/2. Compare with simulation results in a table.


$$\text{Conventional: } R_{out} = \frac{1}{g_{ds4}} \approx 1.8M\Omega$$

$$\text{wide swing: } R_{out} = r_{o5}(1 + (g_{m5} + g_{mb5})r_{o6}) \approx 64M\Omega$$

| <i>Circuit</i> | <i>Simulated</i> | <i>Calculated</i> |
|---------------------|------------------|-------------------|
| <i>Conventional</i> | 1.7M | 85M |
| <i>wide swing</i> | 1.8M | 64M |

 
3. Mismatch

- Perform DC sweep for VMIS1 and VMIS2 from 0 to $\sqrt{1.5} \cdot 3.5m / \sqrt{W \cdot L \cdot 1e12}$ using the code below and set VMIS3 = 0. This models the standard deviation of the mismatch in V_{th} for the current mirror devices. Find the percent change in I_{out} .



I_{out1} vs VMIS1
 
$$\frac{\sigma I_{out1}}{I_{out1}} = \frac{20.394 - 20}{20} \times 100 = 1.97\%$$



I_{out2} vs VMIS2

$$\frac{\sigma I_{out2}}{I_{out2}} = \frac{20.722 - 20}{20} \times 100 = 3.61\%$$


- Analytically calculate the percent change in I_{out} and compare it to the simulation result.

Hint: The voltage change at the gate can be considered as a small signal. Thus, the change in the current can be calculated using the G_m of the circuit. In this case, the circuit can be considered as a cascode amplifier.

$$\frac{\sigma I_{out2}}{I_{out2}} = \frac{g_{m5} V_{mis2}}{I_{out2}} \approx 2.03\%$$

| <i>from simulation</i> | <i>Analytically calculated</i> |
|------------------------|--------------------------------|
| 3.61% | 2.03% |

 - Set VMIS1 = VMIS2 = 0 and perform DC sweep for VMIS3 from 0 to $\sqrt{1.5} \cdot 3.5\text{m} / \sqrt{W \cdot L \cdot 1\text{e}12}$. This models the standard deviation of the mismatch in V_{th} for the cascode devices. Find the percent change in I_{out} .



Iout2 vs VMIS3

$$\frac{\sigma I_{out2}}{I_{out2}} \approx 0 \text{ "as can be seen from the graph"}$$

- Analytically calculate the percent change in I_{out} and compare it to the simulation result.

Hint: The voltage change at the gate can be considered as a small signal. Thus, the change in the current can be calculated using the G_m of the circuit. In this case, the circuit can be considered as a degenerated common source amplifier.

$$\frac{\sigma I_{out2}}{I_{out2}} = \frac{g_{m5}}{1 + g_{m5} r_{06}} V_{mis3} / I_{out2} \approx 0.06\%$$

| <i>from simulation</i> | <i>Analytically calculated</i> |
|------------------------|--------------------------------|
| 0 | 0.06% |

- Which mismatch contribution is more pronounced? Why?
 - The contribution of V_{mis1} and V_{mis2} is much more pronounced due to the fact that they change the value of V_{GS} of mirror devices, which in turn have a one-to-one correspondence with I_D , while the change in V_{mis3} is absorbed by V_{DS} which has a much weaker effect on the current.
- Which design decision is better: setting the same W and L for the mirror and cascode devices? Or using larger W and L for the current mirror devices? Why?

- It can be deduced from the formula of calculating mismatch that larger L and W eventually leads to lower mismatch, so larger L and W is better.